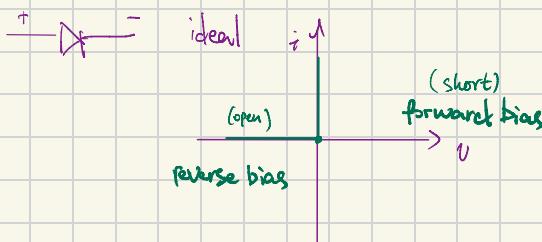





$$A \cos(\omega t) \quad \omega = 2\pi f$$


Diodes



Eg. 3.1

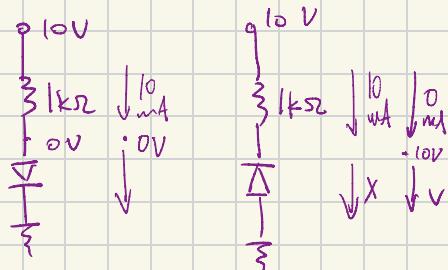

Eg. 3.1

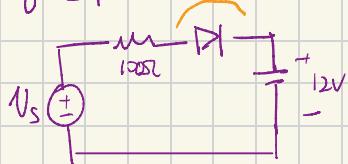

Using a diode circuit to charge a 12-V battery
 $V_s = 24 \cos \omega t$

- a) Find the fraction of each cycle during which the diode conducts


$$\frac{120^\circ}{360^\circ} = \frac{1}{3}$$

- b) the peak value of the diode current


$$i_D = \frac{24 - 12}{10\Omega} = 0.12A$$

- c) the maximum reverse-bias voltage that appears across the diode

$$-24 - (12) = -36V$$

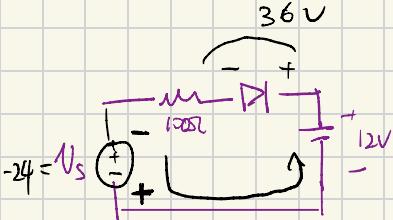


Eg. 3.2

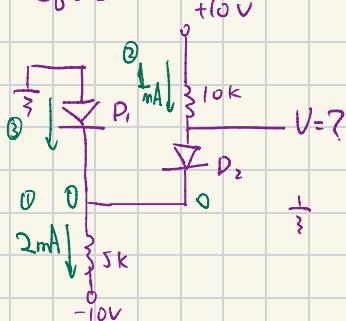

Step 1: 猜 D 导通 or 不导通

$$I_{D1} = 2 - 1 = 1mA$$

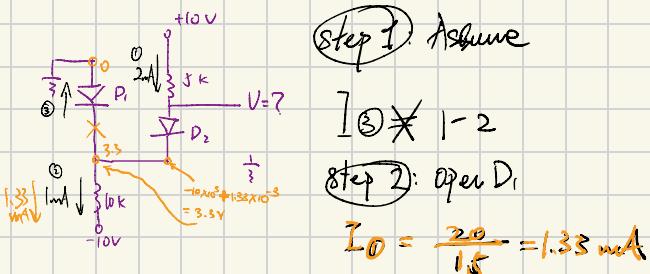


Step 1: Assume

$$I_1 \neq I_2$$

Step 2: Open D₁

$$I_0 = \frac{20}{1.5} = 1.33 \text{ mA}$$



a real diode

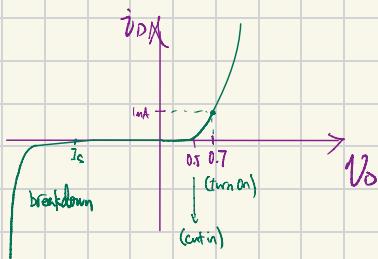


$$i = I_s (e^{V_D/V_T} - 1) \quad V_T = \frac{kT}{q} = 25\text{mV at RT}$$

$$I_s = 10^{-15} \text{ A}$$
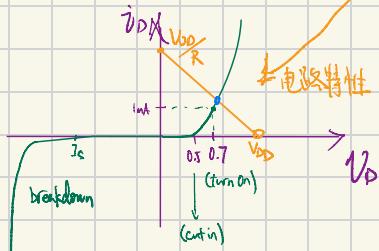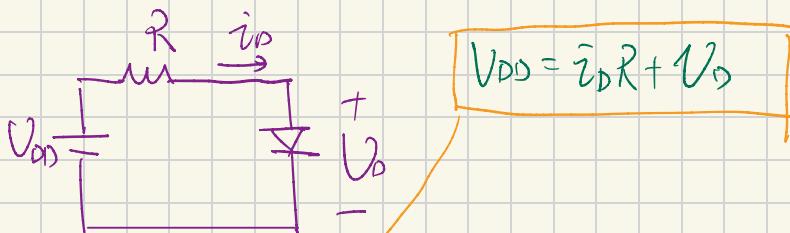
$$i = 10^{-15} (e^{0.7/0.025} - 1) = 1 \text{ mA}$$




Zener diode

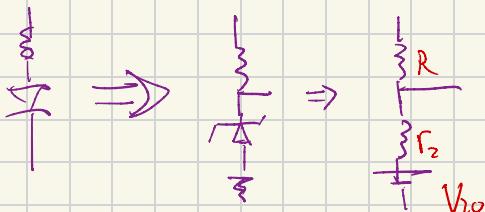

$$I_z = \frac{V_S - V_Z}{R + R_2}$$

Eg.

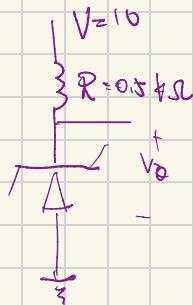


$$V_Z = V_{20} + I_Z \cdot R_Z \Rightarrow 6.8 = V_{20} + I_Z \cdot 0.02$$


find V_{20}

$$I_Z = \frac{10 - 6.7}{0.5 + 20} = 6.35 \text{ mA}$$

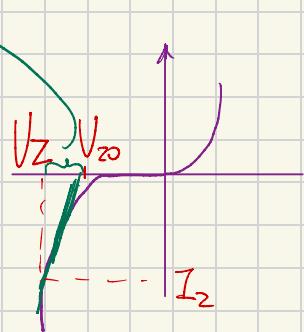
$$V_{20} = 6.7 + 6.35 \text{ mA} \cdot 20 \Omega$$




Peak rectifiers

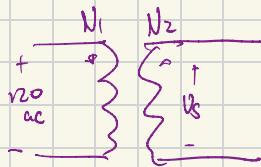


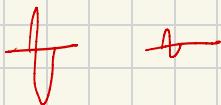
$$\frac{v_{2s}}{v_{1s}} = \frac{N_2}{N_1}$$



Half rectifier




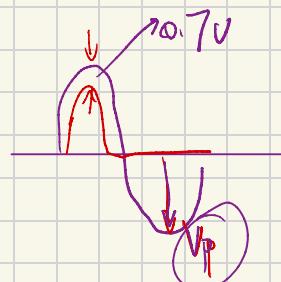


Full rectifier

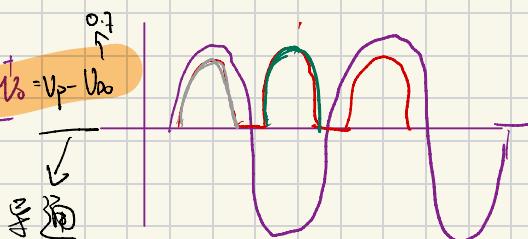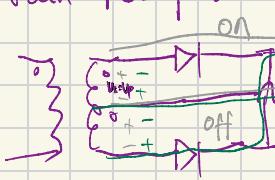

$$(不导通时: U_p + U_p - V_{D0} = 2U_p - V_{D0})$$

§ Bridge rectifier

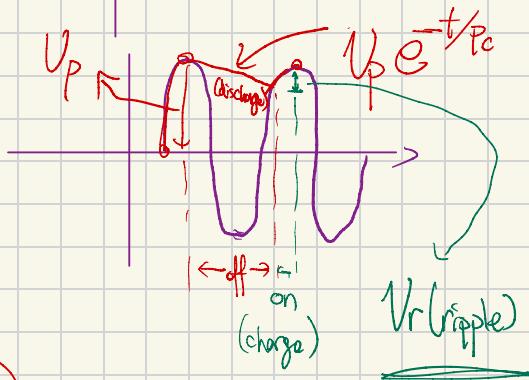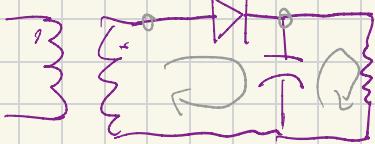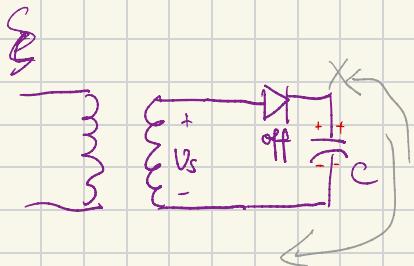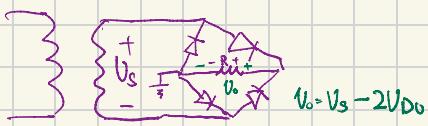


一个周期：放电 V_r = 充电 V_r

$$\Delta Q(\text{discharge}) = \Delta Q(\text{charge})$$

$$\frac{V_r}{R} T = CV_r$$

RLC

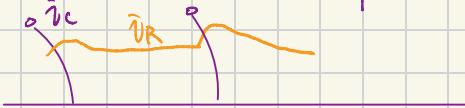
$$\dot{i}_D = \dot{i}_C + \dot{V}_R = C V_p(\omega) \sin(\omega t) + \frac{V_p}{R}$$



$$\begin{aligned} i_D(\text{max}) &= \underline{C V_p(\omega) \omega \Delta t} + \frac{V_p}{R} \\ &= \frac{V_p}{R} \frac{T}{V_r} V_p \omega \sqrt{2 V_r / V_p} \quad \omega = 2\pi f \\ &= \frac{V_p}{R} \left(1 + 2\pi \sqrt{2 V_p / V_r} \right) \end{aligned}$$


$$i_D(\text{AVe}) = \frac{V_p}{R} \left(1 + \pi \sqrt{2 V_p / V_r} \right)$$

3 precision peak rectifier

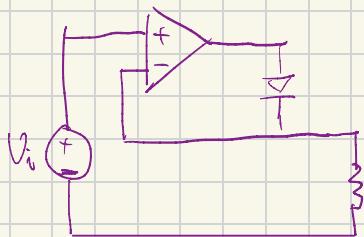


$V_i > 0$, Assume D "on" $\Rightarrow U_o = V_i$

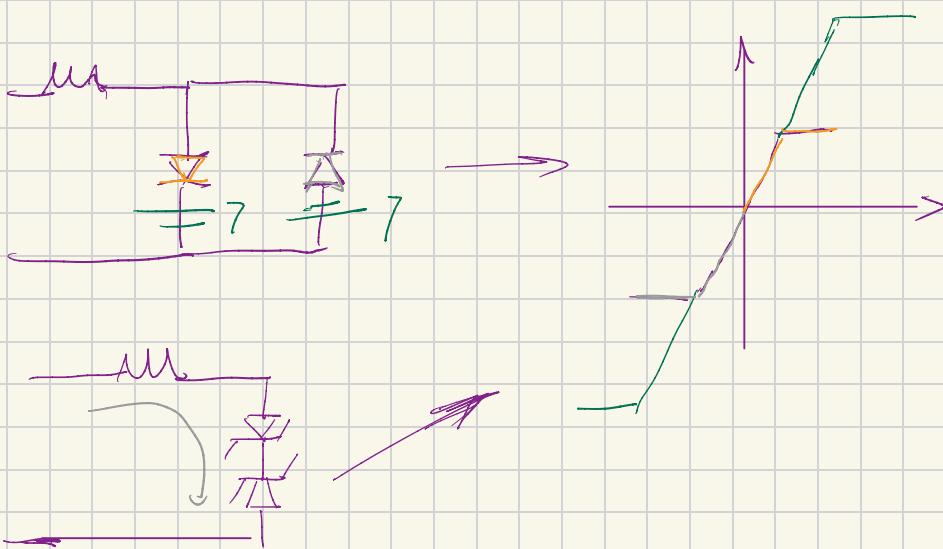$V_i < 0$, Assume D "off" $\Rightarrow U_o = 0$



Clamping Circuit

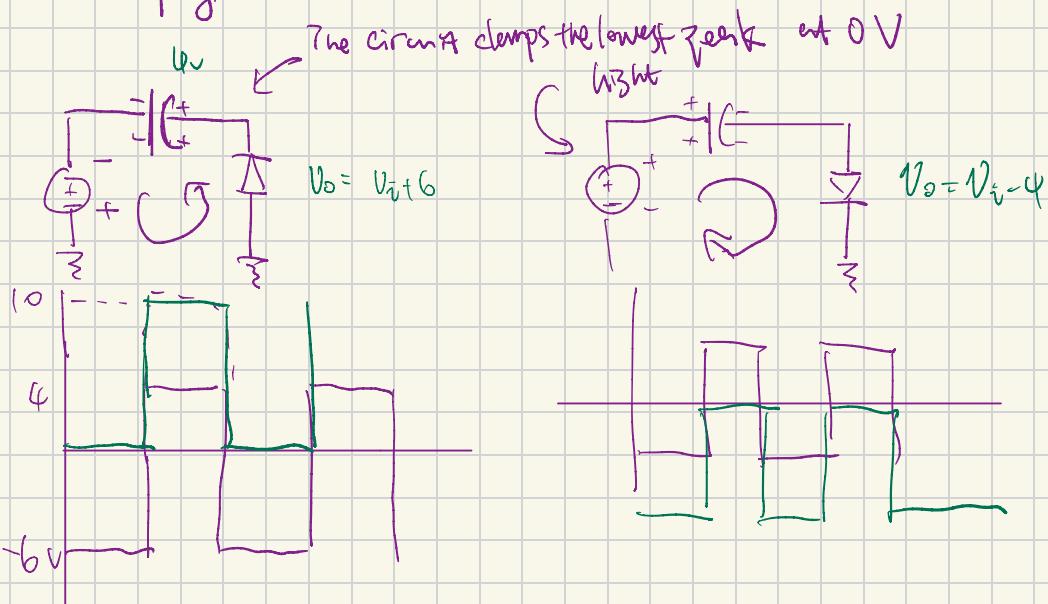

Intrinsic Si $\rightarrow n_i$

$\vec{j} = (\text{free electron}) + (\text{movement of hole})$

n

p

$$n_i = p = n = 10^{10} \text{ cm}^{-3}$$

$$np = n_i^2 = 10^{20} \text{ cm}^{-3} \text{ at RT}$$

Doped Si

n -type Si

Current

drift (under E)

$$\vec{j} = \frac{q}{m} \vec{v} \quad \text{Carrier}$$

$$\vec{j} = q \frac{N}{V} \vec{E} \quad \text{Velocity}$$

$$E_{\text{field}} = 1.6 \times 10^{-9}$$

$$\vec{j} = q_p p \mu_p \vec{E}$$

Diffusion


$$\vec{j} \propto \frac{dn}{dx} \Rightarrow \vec{j}_n = q D_n \frac{dn}{dx}$$

$$U = kT$$

mobility | Diffusion constant

$$\vec{j}_p = q D_p \frac{dp}{dx}$$
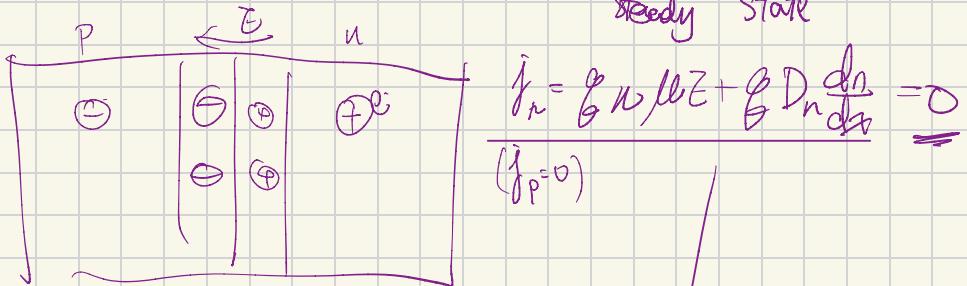
$$\text{Current} \quad \vec{j} = q D_n \frac{dn}{dx} - q D_p \frac{dp}{dx}$$



steady state

$$j_n = g_n \mu E + g_n D_n \frac{dn}{dx} = 0$$


$(j_p = 0)$

$$\frac{U_b}{\pi} \ln \frac{n(x_0)}{n(x_1)} = V(x_2) - V(x_1)$$

$$25mV \ln \frac{10^{16}}{10^5} = V_0 = 0.6V$$

built-in

$$(E=0)$$

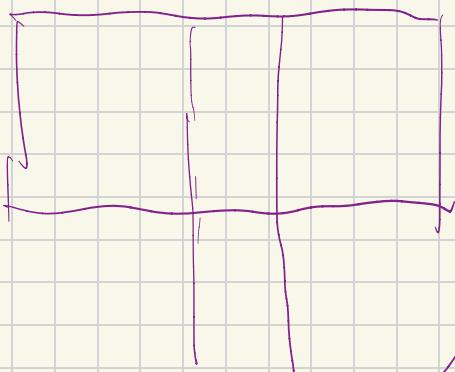

$$j_p = g_p D_p \frac{dp}{dx}$$

$$= g_p D_p \frac{p_{ho}}{\mu_p} (e^{V_{bt}/kT} - 1)$$

$$j_n = g_n D_n \frac{n_{ho}}{\mu_n} (e^{V_{bt}/kT} - 1)$$

$$j = I_s \left(e^{V_{bt}/kT} - 1 \right)$$

$$g_p D_p \frac{p_{ho}}{\mu_p} + g_n D_n \frac{n_{ho}}{\mu_n}$$