

Metal oxide FET transistors

MOSFET transistor DC analysis

MosFET transistor : Small signal analysis

application as an amplifier

application as an amplifier


# MOSFET

金属氧化物半导体场效应晶体管

## ② Metal oxide semiconductor field - Effect - Transistor

(Small, simple)  $\Rightarrow$  larger-scale IC


### S n-channel enhancement-type MOSFET

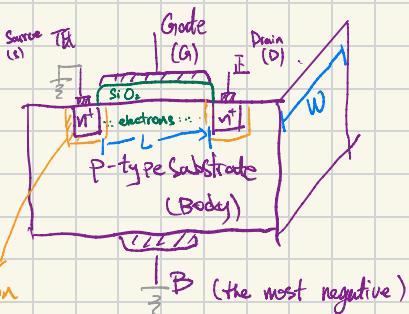

SiO<sub>2</sub>: 绝缘层 (no current goes through, only voltage)

L : channel length

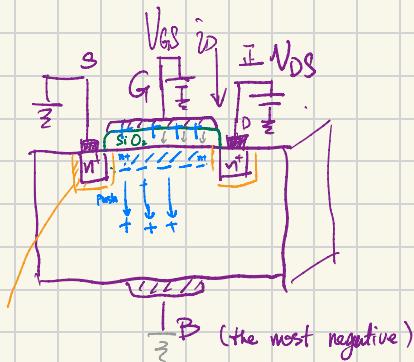"A voltage is applied to Gate to Control the current flow between S and D" (How it work)



operation.

- no gate bias (zero bias), back-to-back diodes,  $i_D = 0$  ( $V_{DS}$  is applied)
- apply a positive  $V_{GS}$ , push holes down to the substrate  $\Rightarrow$  deplete the holes under SiO<sub>2</sub>

further increase  $V_{GS}$   $\Rightarrow$  inverse P to n under SiO<sub>2</sub>



The value of  $V_{GS}$  at which a just sufficient number of mobile electrons accumulated in the channel is called the threshold voltage.

$$U_{th} \text{ or } U_t = 0.2 \text{ mV}$$


$$i_D = j_n = q n \mu_n E$$

electron:  $n = n_0 e^{\frac{(V_{GS} - U_{th})}{kT}}$

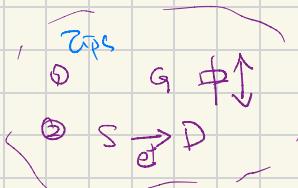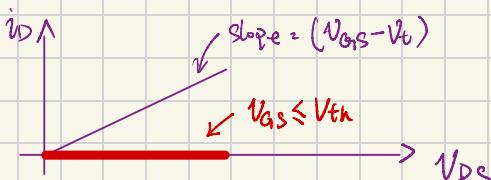
Electric Field =  $\frac{V_{GS}}{L}$  (quadrive)



## ② § n-channel enhancement-type MOSFET

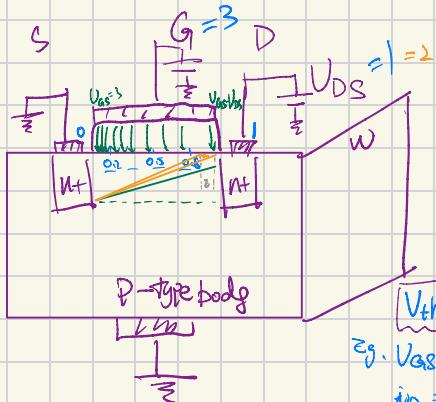

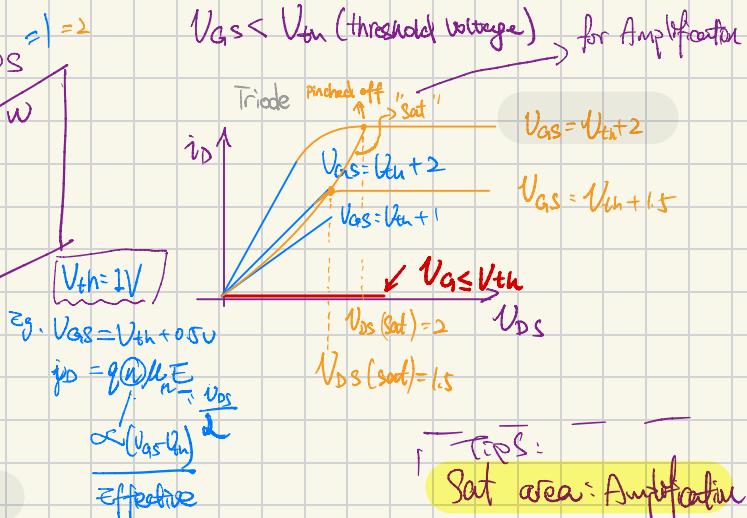The voltage between G and points along the channel decrease from  $V_{GS}$  at S end to  $V_{GS} - V_{DS}$  at D end.



Eventually, when  $V_{GS} - V_{DS} = V_t$ .


the channel depth at 0 is almost zero  $\Rightarrow$  the channel is pinched off

工作在饱和区:  $V_{DS} > [V_{DS}(\text{sat}) = V_{DS} - V_{th}]$

OR 有  $V_{GS} - V_{th} \geq V_{DS}$  ( $G$  离  $D$ )

### § 4.16 Derivation of the $i_s - V_{DS}$ relationship

Consider "Triode" region

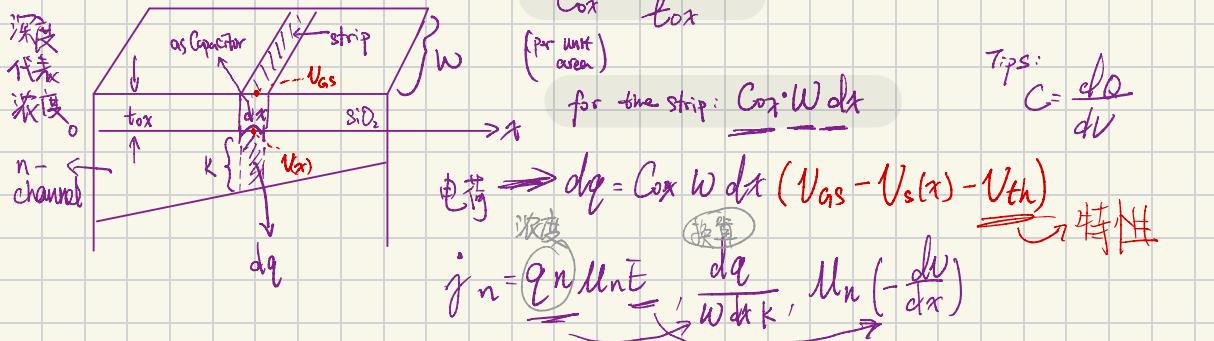

$$\text{Electron Current} \rightarrow j_n = q n \mu_n E = \frac{dq}{W dx k} \mu_n \left( -\frac{dV}{dx} \right)$$

(b)

$$i = j_n kW = q n \mu_n E = \frac{dq}{W dx k} \mu_n \left( -\frac{dV}{dx} \right)$$

$$i_D = j_n kW = \frac{dq}{dx} \mu_n \left( \frac{dV}{dx} \right) = \mu_n C_{ox} W (V_{GS} - V_{th}) \frac{dV}{dx}$$

$$\int_0^L i_D dx = \mu_n C_{ox} W \int_0^{V_{DS}} \underbrace{[(V_{GS} - V_{th}) - V_{DS}]}_{\text{const}} dV$$

$\uparrow$   
const

$$i_D L = \mu_n C_{ox} W \left[ (V_{GS} - V_{th}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \Rightarrow$$


$$i_D = \frac{\mu_n C_{ox} W}{2} \left[ (V_{GS} - V_{th}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$\frac{-V_{DS}(V_{DS}-V_{th})}{2}$  slope

Consider "saturation"

$$i_D = \mu C_{ox} \left( \frac{w}{l} \right) \left[ (V_{GS} - V_{th}) V_{DS(\text{sat})} - \frac{1}{2} V_{DS(\text{sat})}^2 \right]$$
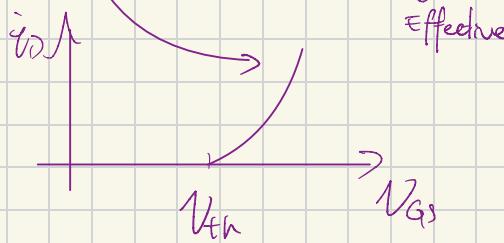
$$= \frac{1}{2} \mu_n C_{ox} \left( \frac{w}{l} \right) (V_{GS} - V_t)^2$$



$$\boxed{V_{DS(\text{sat})} = (V_{GS} - V_t)}$$

$$\boxed{V_{GS} - V_t \equiv V_{ov} \text{ (overdrive)}}$$

Consider "Boundary" (把 Set point 连起来)

$$\boxed{i_D = \frac{1}{2} \mu C_{ox} \left( \frac{w}{l} \right) V_{DS}^2}$$

$$\boxed{V_{ov} = V_{GS} - V_{th}}$$

Eg. for  $t_{ox} = 8 \text{ nm}$ ,  $\mu_n = 450 \text{ cm}^2/\text{V.s}$   $V_t = 0.7 \text{ V}$

a) find  $C_{ox} = \frac{C_0 x}{t_{ox}} = \frac{3.45 \times 10^{-11}}{8 \times 10^{-9}} = 4.32 \times 10^{-3} \text{ F/m}^2$

$$\mu_n C_{ox} = 19.4 \text{ MA/V}^2$$

b)  $\frac{W}{L} = 8 \text{ \mu m} / 0.8 \text{ \mu m}$ , for "Sat" with  $I_D = 100 \text{ mA}$ ,  $V_{GS} = ?$   $V_{DS(\text{min})} = ?$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$100 \text{ mA} = \frac{1}{2} \cdot \left( \frac{10}{1} \right) 19.4 \frac{\text{mA}}{\text{V}^2} (V_{GS} - 0.7)^2 \Rightarrow V_{GS} = 1.02 \text{ V}$$

$$\text{Sat} \rightarrow V_{DS} > V_{GS} - V_t \Rightarrow \underline{\underline{V_{DS(\text{min})} = 0.32 \text{ V}}} \quad \checkmark$$

c) for a 1000-SL resistor, for very small  $V_{DS}$

$$1000 = R_{DS} = \frac{V_{DS}}{I_D} = \sqrt{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)}$$


$$\therefore V_{GS} = 1.22$$

Tips: BY


$$I_D = \frac{\mu_n C_{ox} W}{2} [(V_{GS} - V_t)(V_{DS} - \frac{1}{2} V_{DS}^2)]$$

2倍割掉 很好



## ② n-channel (enhancement-type) MOSFET


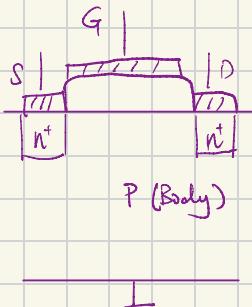


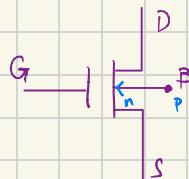circuit model  $n \rightarrow n\text{-channel}$   
 $p \rightarrow \text{Body}$



电从S出发, 从D流出

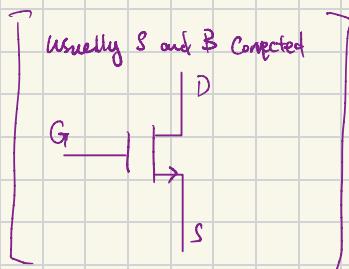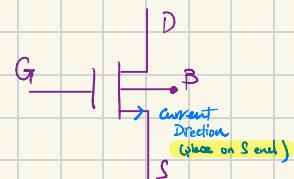


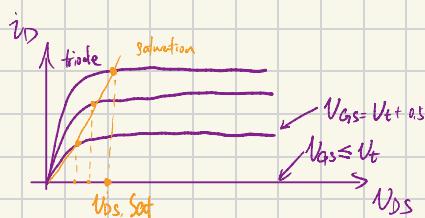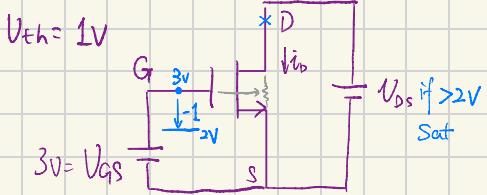


$$\left\{ \begin{array}{l} \text{Sat} \Rightarrow i_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) (V_{GS} - V_t)^2 \\ \text{triode} \Rightarrow i_D = \mu C \left( \frac{W}{L} \right) [ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 ] \end{array} \right.$$

改變 R 性質  
 $V_{GS} \uparrow R_L$   
 $i_D = V_{DS}$  (linear 線性)
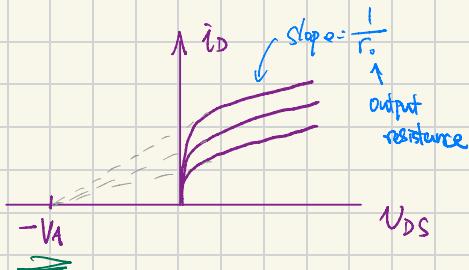
### § 4.2, Channel-length modulation effect (Early Effect)


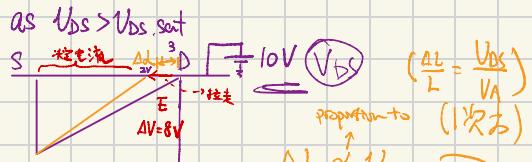
$$R_o = \frac{1}{\left( \frac{\partial i_D}{\partial V_{DS}} \right)} = \frac{1}{\frac{i_D}{V_A}} \quad \text{no early effect}$$




$$i_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$i_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) \left( 1 - \frac{\Delta I}{I_D} \right) (V_{GS} - V_t)^2$$

$$i_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) \left( 1 + \frac{V_{DS}}{V_A} \right) (V_{GS} - V_t)^2$$

$V_A$ : Constant

### § P-channel


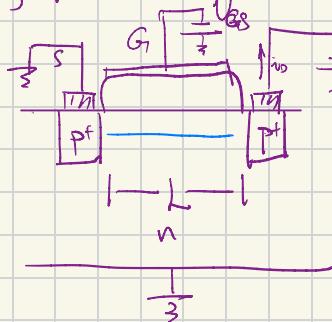


$$V_{GS} - V_{DS} = V_t$$


pinched off

$$V_t = -1 \text{ V}$$


$V_{DS} = V_t$  just forms  
a P-channel

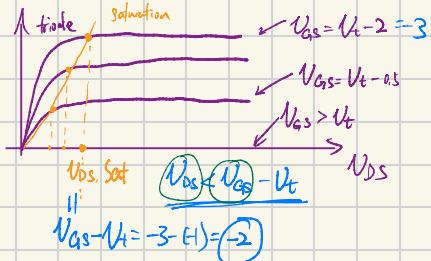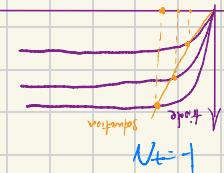


(Sat)  $V_{DS} < V_{GS} - V_t$

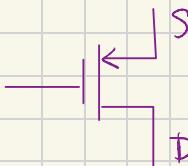
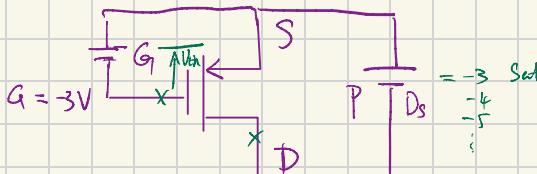
$$i_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$



### § 4.2

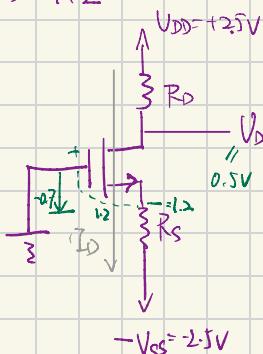

$$R_D = ? \quad R_S = ?$$

$$\text{So that } I_D = 0.4 \text{ mA}, V_D = 0.5 \text{ V}$$

$$(V_{th} = 0.7 \text{ V}, \mu C = 100 \text{ mV/V}, L = 1 \text{ mm}, W = 32 \text{ mm})$$

n-channel


$$\underline{\text{sat}} \Rightarrow i_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$400 = \frac{1}{2} \cdot 100 \left( \frac{32}{1} \right) (V_{GS} - 0.7)^2 \Rightarrow V_{GS} = 1.2 \text{ V}$$

$$R_S = \frac{-1.2 - (-2.5)}{0.4} k\Omega = 3.25 k\Omega$$

$$R_D = \frac{2.5 - 0.5}{0.4} = 5 k\Omega$$

Eq. 4.3

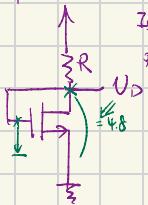

$$ID = 8 \text{ mA} \quad (V_t = 0.6 \text{ V}, \mu C = 200 \text{ nA/V}^2, L = 0.8 \text{ um}, W = 4 \text{ um})$$

$$R = ? \quad V_D = ?$$


Check Sat  $\because$  In Source wire  $\therefore$  Sat

$$i_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$8 = \frac{1}{2} 200 \left( \frac{4}{0.8} \right) (V_{GS} - 0.6)^2 \Rightarrow V_{GS} = 1 \text{ V}, V_D = 4.8 \quad \checkmark$$

$$R = \frac{3.1}{0.08} = 38.75 \text{ k}\Omega \quad \checkmark$$

Eq. 4.4

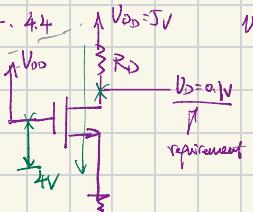

$$V_t = 1 \text{ V}, \mu C \left( \frac{W}{L} \right) = 1 \text{ mA/V}^2, R_D = ?, V_D = 0.1$$

Check Sat?

No, Triode

$$\therefore i_D = \mu C \left( \frac{W}{L} \right) [(V_{GS} - V_t)(V_{DS} - \frac{1}{2} V_{DS}^2)]$$

$$= 1 \cdot [(5-1)(0.1) - \frac{1}{2}(0.1)^2]$$

$$= 0.375 \text{ mA}$$


$$R_D = \frac{5-0.1}{0.375} = 12.4 \text{ k}\Omega$$

Eq. 4.5

$$V_{DD} = 10 \text{ V}$$

$$V_t = 1 \text{ V}, \mu C \left( \frac{W}{L} \right) = 1 \text{ mA/V}^2$$

guess, Sat

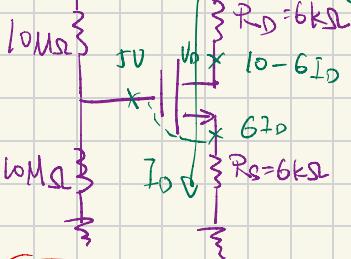

$$I_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$


$$I_D = 0.5 (5 - 0.5 - 1)^2$$

$$I_D = 0.8 \text{ mA} \quad \underline{\underline{0.8 \text{ mA}}} \quad \text{or} \quad \underline{\underline{0.5 \text{ mA}}}$$

$$\text{or } 6ID = 6 \times 0.8 = 5.34 \quad \times$$


$$6ID = 6 \times 0.5 = 3 \text{ V} \quad \checkmark$$

$$V_D = 10 - 6 \times 0.5 = 7$$

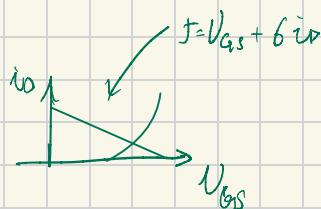

MSL 可为持信号 (AC 信号)  $T > (5-1)$   $\checkmark$

Eg. 4.5

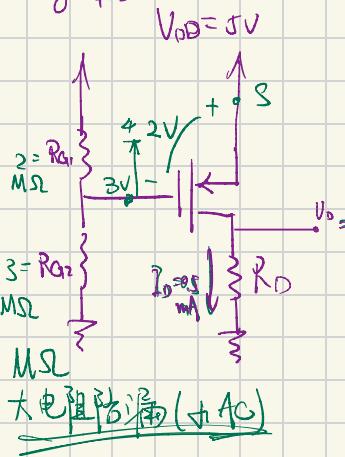

Sat? Gated Drain FET

$$k' = \mu C$$

Design the circuit

So that the MOSFET is in "sat" with  $I_D = 0.5mA$  &  $I_D = 3V$

$$(V_{th} = 1V, k'_p (\frac{W}{L}) = 1mA/V^2)$$

P-channel

$$i_D = \frac{1}{2} k'_p \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 \quad V_{GS} - V_t = \pm 1V$$

$$0.5 = \frac{1}{2} \cdot 1 \cdot (V_{GS} + 1)^2 \Rightarrow V_{GS} = -2V, 0V$$

$$R_D = \frac{3}{0.5} = 6k\Omega$$

What is the largest  $R_D$  that can have while maintaining "Sat"

$R_D$ ?


$$R_D = \frac{4}{0.5} = 8k\Omega$$

Eg. 4.7

$$k'_n (\frac{W}{L})_n = k'_p (\frac{W}{L})_p = 1mA/V^2 \quad U_{tn} = -U_{tp} = 1V$$

Find  $i_{DP}$ ,  $i_{DN}$  for  $V_i = 0, 2.5, -2.5V$

CMOS

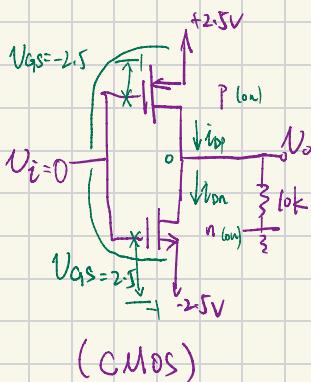

by

$$\frac{-2.5 - (-1)}{2.5 - 1} (V_{GS} - V_t) \Rightarrow i_{DP} = i_{DN} \Rightarrow V_o = 0$$

(Sat)

$$i_{DN} = \frac{1}{2} k'_n \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$$


$$= \frac{1}{2} \cdot 1 \cdot (2.5 - 1)^2 \Rightarrow i_{DN} = 1.125mA$$

$$i_{DP} = 1.125mA$$



Transmission Gate (信号选择)

$$\begin{cases} r \rightarrow \frac{1}{2} \\ \parallel \rightarrow 0 \end{cases}$$


$$\boxed{V_{GS} > |I_{th}| \text{ 通过}}$$

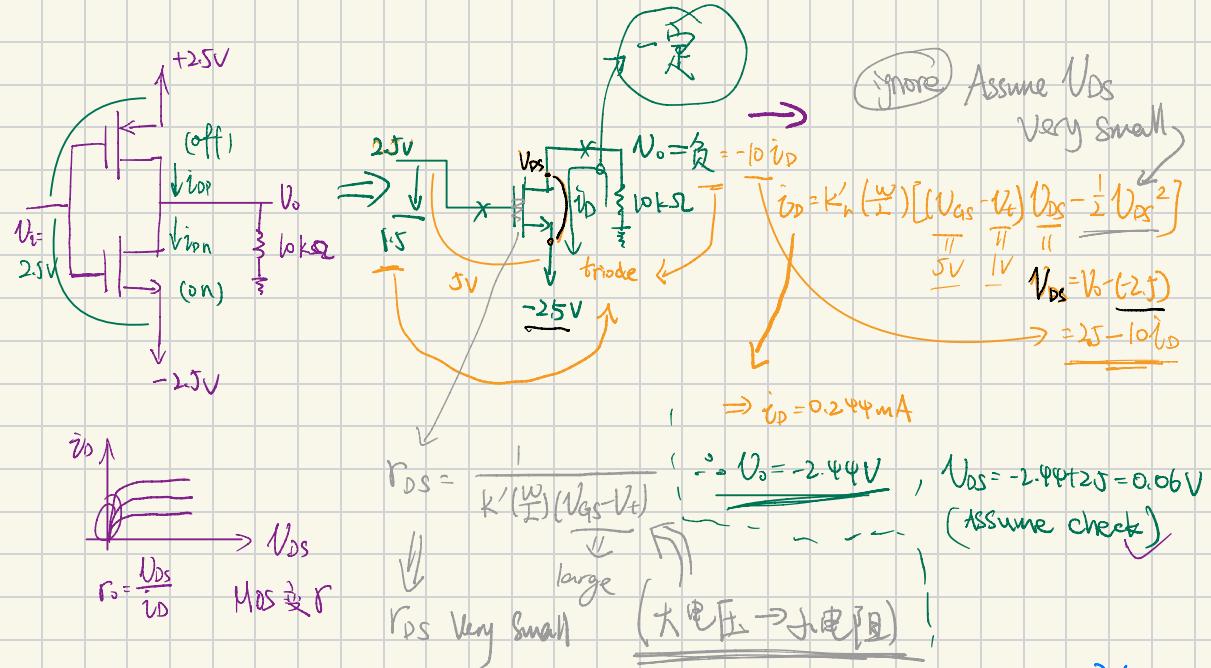
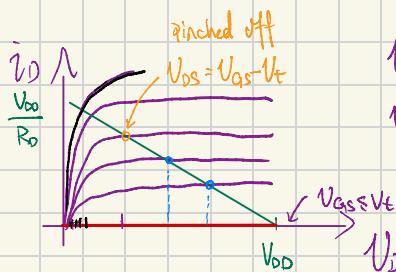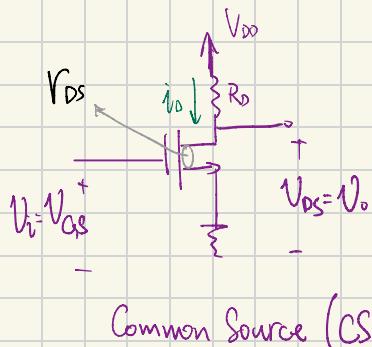
## § 4.4 Large-Signal operation - the transfer characteristic


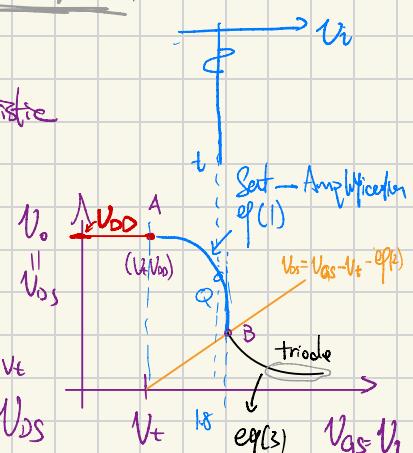
$$V_{DD} = i_D R_D + V_{DS} \quad (\text{load line})$$



$$(eq1) = V_{DD} - \frac{1}{2} \mu C \left( \frac{w}{l} \right) (V_{GS} - V_t)^2$$

triode:

$$(eq2) V_o = V_{DD} - R_D \mu C \left( \frac{w}{l} \right) \left( V_{GS} - V_t \right) V_{DS} - \frac{V_{DS}^2}{2}$$

$$V_o = V_{DD} - R_D \mu C \left( \frac{w}{l} \right) \left[ (V_i - V_t) V_o - \frac{V_o^2}{2} \right]$$

$$\left[ 1 + R_D \frac{1}{R_{DS}} \right] V_o = V_{DD} \quad \text{Ignore } L$$

$$V_o = V_{DD} \frac{R_{DS}}{R_D + R_{DS}}$$

B point can be solved from eq(1) and eq(2)

Amplification.

AC gain

$$A_V = \frac{\partial V_o}{\partial V_t} \Big|_Q = -\mu C \left( \frac{w}{I} \right) (V_{GS} - V_t) R_D$$



$$\text{+} \quad \sqrt{I_D} = \sqrt{\frac{1}{2} \mu C \left( \frac{w}{I} \right) (V_{GS} - V_t)} \\ = -R_D \sqrt{\frac{2 I_D}{\mu C \left( \frac{w}{I} \right)}} \quad \xrightarrow{\text{DC}} \quad \left( A_V \propto \sqrt{I_D} \right)$$

(24)

§ 4.4

Eg. 4.8 Consider a CS circuit
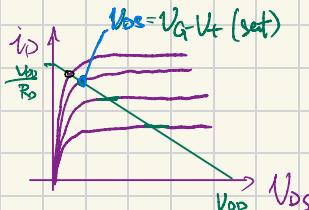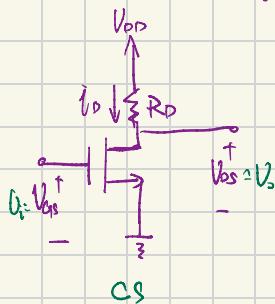
$$I_t = 1/V, \mu C \left( \frac{w}{I} \right) = 10 \text{ A/V}, R_D = 18 \text{ k}\Omega, V_{DD} = 10 \text{ V}$$




$$V_{DS} = V_{DD} - i D R_D \quad (\text{load line})$$

$$\begin{aligned} (SOL) \quad & V_o = V_{DD} - \frac{1}{2} \mu C \left( \frac{w}{I} \right) (V_{GS} - V_t)^2 - zq(4) \\ & = 10 - \frac{1}{2} (10-1)^2 / 18 \end{aligned}$$

$$V_o = V_t - 1$$

Amplification.

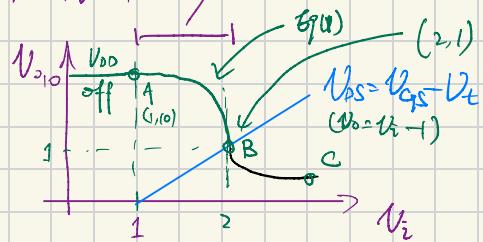

Vt

$$\Rightarrow V_o = 1, V_t = 2$$

B (2,1)


$$V_o = V_{DD} - \mu C \left( \frac{w}{I} \right) [(V_t - 1)V_o - \frac{1}{2} V_o^2] R_D$$

$$V_o = 10 - [(10-1)V_o] \times 18$$

$$V_o = 0.061 \text{ V}$$

放大? (Amplification)

上段

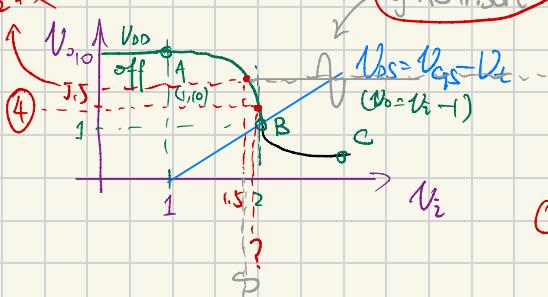

由 Ac insert

Q


① Design  $V_o = 4V \Rightarrow V_i$  ?

$$V_o = V_{DD} - \frac{1}{2} M C \left( \frac{W}{L} \right) (V_i - V_T)^2 R_D$$

$$4 = 10 - \frac{1}{2} (V_i - 1)^2 \cdot 18$$

$$V_i = 1.816V$$

② How to know  $A_v$  ?

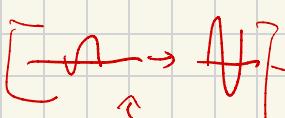

$$A_v = \frac{\partial V_o}{\partial V_i} = - \frac{M C \left( \frac{W}{L} \right) (1.816 - 1)}{18}$$

$\therefore$  有负相反

## § 4.5 MOSFET DC Bias

bias stability (set)

$$\therefore \Rightarrow A_v = - M C \left( \frac{W}{L} \right) (V_{GS} - V_T) R_D \Rightarrow - R_D \sqrt{2 M C \left( \frac{W}{L} \right) I_D}$$

$$\boxed{I_{D0} = \frac{1}{2} M C \left( \frac{W}{L} \right) (V_{GS} - V_T)^2}$$

$\frac{d}{dT}$

$$\boxed{\sqrt{\frac{2 I_{D0}}{M C \left( \frac{W}{L} \right)}} = (V_{GS} - V_T)}$$

$$\therefore A_v \propto \sqrt{I_D}$$

Stability?  $\Rightarrow \Delta T$  会 affect  $\Delta I_D$ ,  $A_v$  会改变

( $\propto C$  与  $T$  有关)

$\Downarrow$

$\Delta K'$  in a batch  $\Rightarrow \frac{\Delta I_D}{I_D}$


①

as small as possible is good  $\Rightarrow$  Stability  $\uparrow$

§ 4.5


$\rightarrow R_S \rightarrow \text{Stability} \uparrow$

fixed  $V_{GS}$

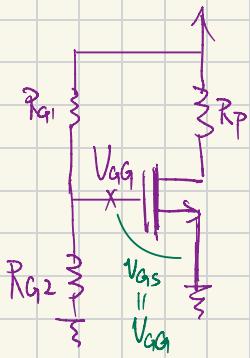


$$V_{GG} = V_{DD} + \frac{R_{G2}}{R_{G1} + R_{G2}}$$
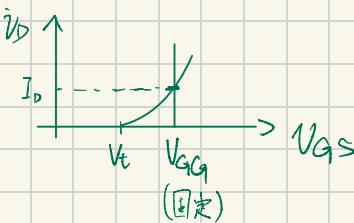
$$\text{Sat. } i_D = \frac{1}{2} k_C \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$




REPLACE  
MOS

$k' - K'$  changed

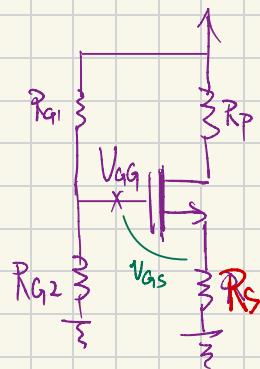


$$V_{GSf} = V_{GS} + i_D R_S$$

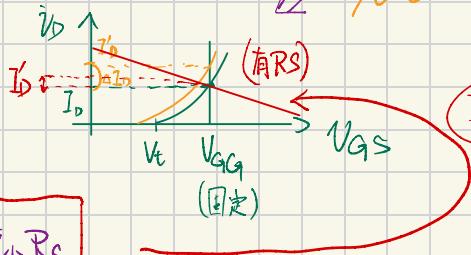

$\therefore R_S \rightarrow \lambda \Rightarrow \text{Increase Bias Stability}$

$$K' \uparrow \Rightarrow i_D \uparrow \Rightarrow V_{GS} \uparrow \xrightarrow{+R_S} A i_D \downarrow$$

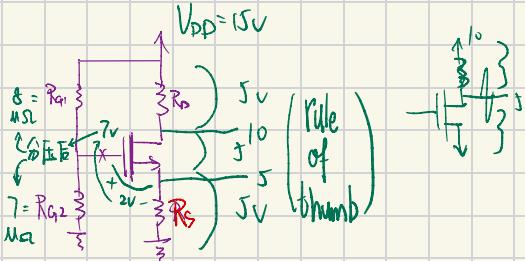Eg. 4.9 Design to have  $I_D = 0.5 \text{ mA}$  ( $V_t = 1 \text{ V}$ ,  $K'(\frac{W}{L}) = 1 \text{ mA/V}^2$ ,  $V_{DD} = 15 \text{ V}$ )




(Sol.):

$$R_D = 10 k_S L = R_S$$

$$(SOL) 0.5 = \frac{1}{2} 1 \cdot (V_{GS} - 1)^2$$

$$V_{GS} = 2$$

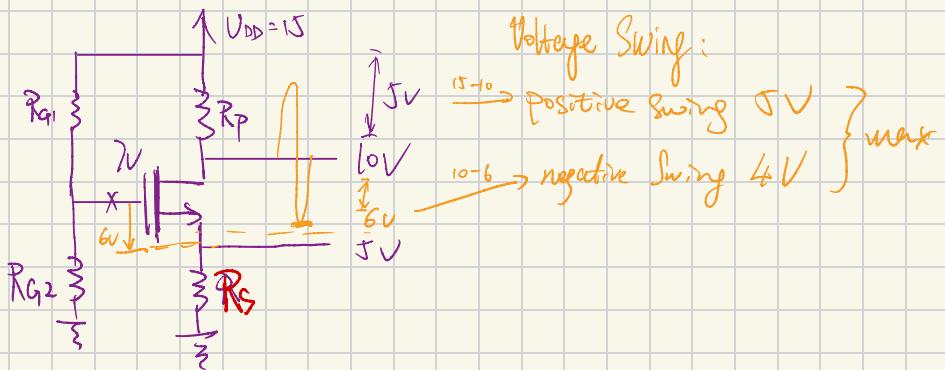

§ Replace by another, Same  $K'(\frac{W}{L})$  but  $V_t = 1.5V$


$$i_D = \frac{1}{2} \cdot 1 \cdot (V_{GS} - 1.5)^2 \quad (1)$$

$$V_{OA} = V_{GS} + i_D R_S \quad (2)$$

$$I_D = 0.455 \text{ mA}$$

$$\frac{A I_D}{I_D} = 9\%$$

§ 4.5.3

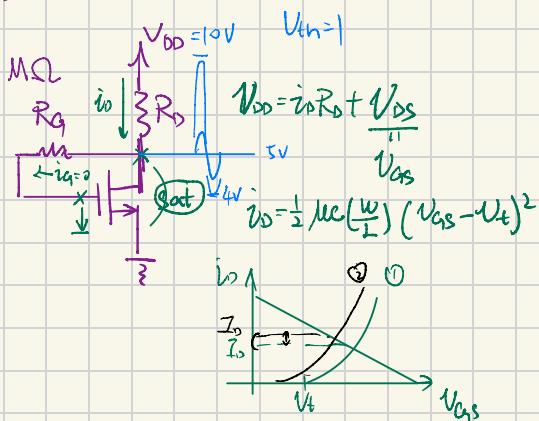

If  $K' \uparrow \Rightarrow i_D \uparrow = V_{GS} \downarrow \Rightarrow \Delta i_D \downarrow$

但是


Swing 不平衡

Negative Swing 太小, R 有  $V_{tH}$


$\therefore R_G$  increase bias stability  
 (negative feedback)

§ 4.5.4
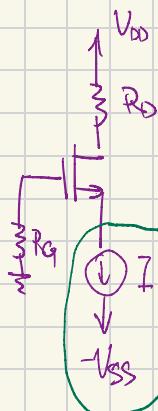
## Biasing Using a Constant-current Source



### Current Mirror

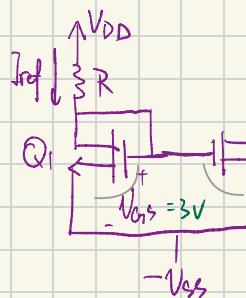

$$I_{ref} = \frac{1}{2} K' \left( \frac{w}{l} \right) (V_{GS} - V_t)^2$$

$$\frac{V_{DD} - V_{GS} - (-V_{SS})}{R} = I_{ref}$$



} Solve  $I_{ref} = f(R)$

$$I = \frac{1}{2} K' \left( \frac{w}{l} \right)_2 (V_{GS} - V_t)^2$$

$$\frac{I}{I_{ref}} = \frac{\left( \frac{w}{l} \right)_2}{\left( \frac{w}{l} \right)_1} = 1$$

} (matched)

## § 4.6 Small Signal operation.

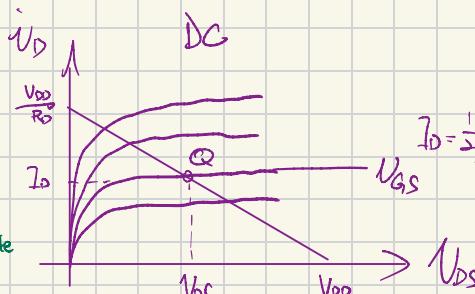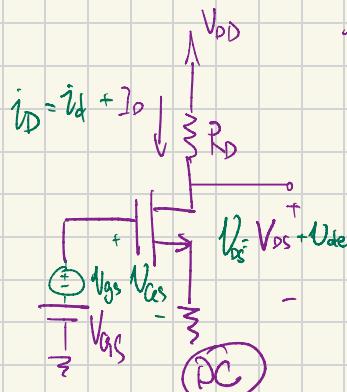

$$V_{DD} = I_0 R_D + V_{DS0}$$

$$Ac analysis \Rightarrow i_{D0} = \frac{1}{2} Kc \left( \frac{w}{l} \right) (V_{GS0} - V_t)^2$$

$$= \frac{1}{2} Kc \left( \frac{w}{l} \right) [(V_{GS0} - V_t)^2 + 2(V_{GS0} - V_t)(V_{DS0} + V_t) + (V_{DS0} + V_t)^2]$$

} Assume  $V_{DS} \ll 2(V_{GS0} - V_t) \Rightarrow$  Small signal Approximation

include DG  
AC


$$= I_D + \underbrace{MC\left(\frac{W}{L}\right)(V_{GS} - V_t)V_{GE}}_{i_d} \quad \text{AC Sin}$$

Define: transconductance

$$( \text{typically } g_m = 1 \text{ mA/V} ) \quad g_m = \frac{i_d}{V_{GE}} = MC\left(\frac{W}{L}\right)(V_{GS} - V_t) = \frac{\partial i_d}{\partial V_{GS}} \quad \text{OR}$$

$$\overline{I_D} = \sqrt{\frac{1}{2}MC\left(\frac{W}{L}\right)(V_{GS} - V_t)} \quad = \sqrt{\frac{1}{2}MC\left(\frac{W}{L}\right)i_d}$$

$$i_d = g_m V_{GE}$$

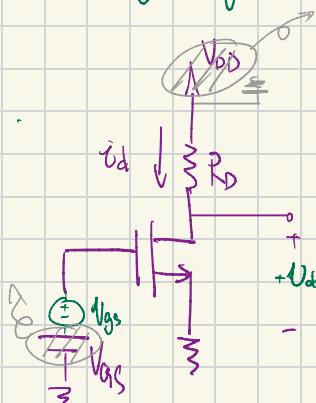


$$\begin{aligned} V_{DS} &= V_{DD} - i_D R_D \\ V_{DS} + V_{DGE} &= V_{DD} - (I_D + i_d) R_D = V_{DD} - I_D R_D - i_d R_D \\ \Rightarrow V_{DGE} &= -i_d R_D \end{aligned}$$

ignore DC


AC : Short all DC Voltage

§ Small-signal equivalent circuit Model  $i_d = g_m V_{GE}$

Hybrid- $\pi$  model

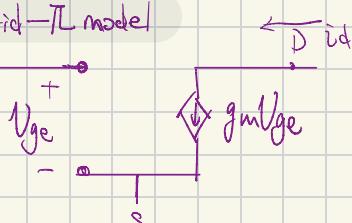

E.g.


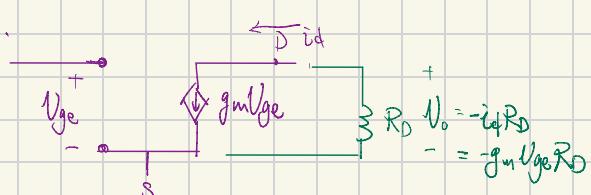


§ channel-length Modulation Effect (Early Effect)

$$I_D = \frac{1}{2} \mu C \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 = \frac{1}{2} \mu C \left(\frac{W}{L}\right) \left(\frac{1}{1 - \frac{V_D}{V_A}}\right) (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} \mu C \left(\frac{W}{L}\right) \left(1 + \frac{V_D}{V_A}\right) (V_{GS} - V_t)^2$$

AJ  $\propto V_{DS}$

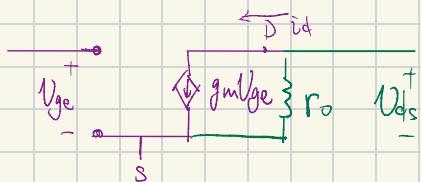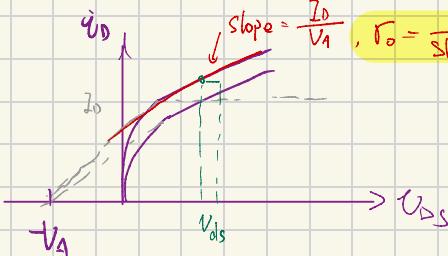

$$i_D = i_D(V_{GS}, V_{DS})$$

$$\frac{di_D}{dV_{GS}} = \frac{\partial i_D}{\partial V_{GS}} + \frac{\partial i_D}{\partial V_{DS}} \frac{\partial V_{DS}}{\partial V_{GS}}$$

$$i_{dS} = g_m V_{Ge} + \frac{1}{r_o} I_D$$


$$i_{dS} = g_m V_{Ge} + \frac{V_{DS}}{r_o}$$

Step: DC analysis  $\rightarrow g_m$  (A<sub>c</sub>放大倍数)  $\rightarrow$  Early effect equation &  $r_o$  图

(No Early Effect)  
Consider

### § 4-6

Ex.

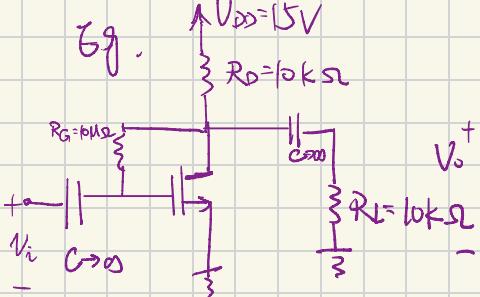


$$V_{DS} = 15V, \mu C \left(\frac{W}{L}\right) = 0.25mA/V^2, V_A = 50V$$

final  $V_o/V_i$  &  $R_i$

(So)


DC analysis:

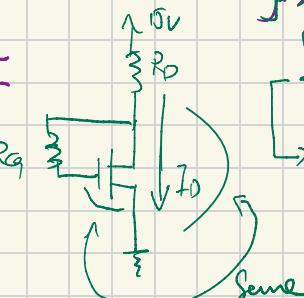

$$\begin{cases} I_D = \frac{1}{2} \mu C \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 \\ 15 = I_D R_D + V_{GS} \quad (\because V_{DS} = V_{GS}) \end{cases}$$

$$\rightarrow I_D = 1.06mA, V_{GS} = 4.4V$$


$$R = 10k\Omega$$

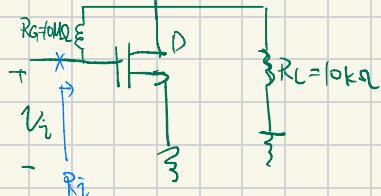

$$r_o = \frac{V_A}{I_D} = \frac{50}{1.06mA} = 47k\Omega$$

$$g_m = \mu C_s \left( \frac{w}{L} \right) (V_{GS} - V_t) = 0.725 \mu A/V$$

AC analysis:

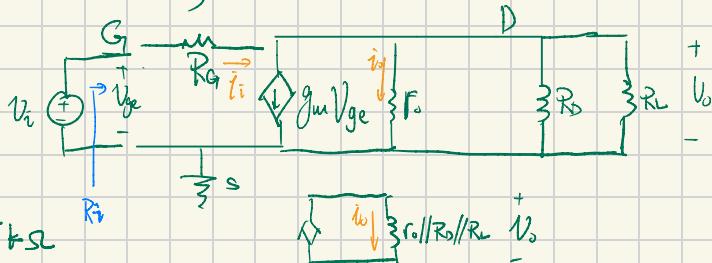

$$\frac{i_o}{V_o} = \frac{1}{R_d // R_o // R_L}$$

$$i_o = i_d - g_m V_{ge}$$

Assume  $i_d \ll g_m V_{ge}$  ( $\because R_d = 10M\Omega$ )

$$i_o = -g_m V_{ge}$$

$$\frac{V_o}{V_i} = -g_m (r_o // R_d // R_L) \Leftarrow \frac{V_o}{V_i} = -g_m V_{ge} (r_o // R_d // R_L)$$

$$\frac{V_o}{V_i} = -g_m (r_o // R_d // R_L)$$

$$= -3.3 \%$$

$$R_i = \frac{V_i}{i_i} = \frac{V_i R_d}{4.3 V_i} = \frac{R_d}{4.3} = 2.33 M\Omega$$

$$\frac{V_i - V_o}{R_d} \quad (V_o = 4.3)$$

( $R_i$  很大, why?)  $\Rightarrow$   $\therefore$  电源也有内电阻,


$\therefore R_s$  与  $R_i$  分压,  $R_i$  分大电压正常 circuit 工作

Proof:

$$\frac{1}{g_m} \ll \frac{V_{ge}}{i_i} \quad (V_{ge} = V_d)$$

$$1.3 k\Omega \ll (R_i = 2.3 M\Omega)$$

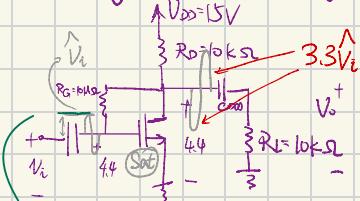
The largest input Voltage Swing? keep Sat



$$\begin{aligned} & 4.4 + V_i \\ & 4.4 - 3.3V_i \\ & 4.4 - 3.3V_i \geq 4.4 + V_i - V_t \\ & V_i \leq 0.34V \end{aligned}$$


O 26

## Small-Signal operation

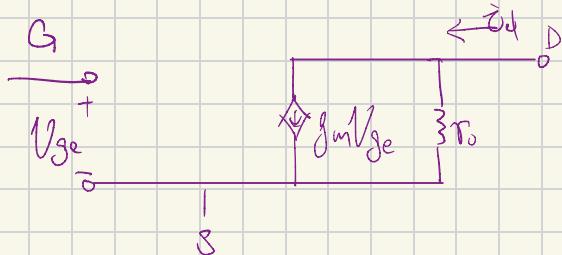
→ Hybrid- $\pi$  model

$$\begin{aligned} j_m &= \mu C \left( \frac{w}{L} \right) (V_{gs} - V_{th}) \\ &= \sqrt{2 \mu C \left( \frac{w}{L} \right) I_D} \end{aligned}$$

→ T-model

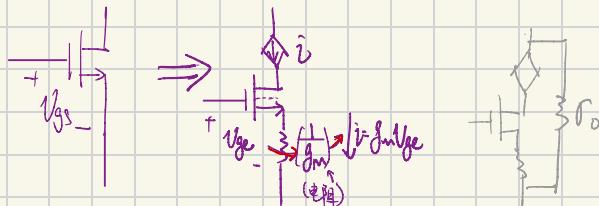


Ex. 4.10

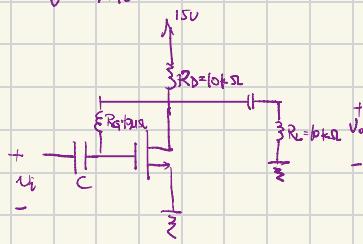

$$\mu C \left( \frac{w}{L} \right) = 0.25 \text{ mA/V}^2, V_A = 50 \text{ V}$$

AC analysis

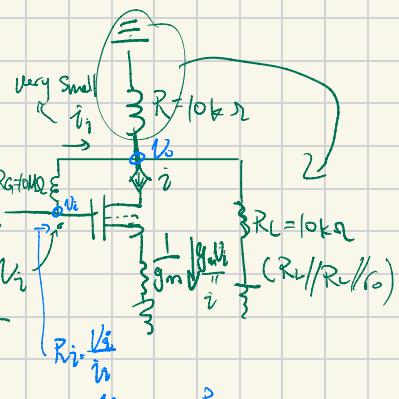

DC analysis:

$$\begin{cases} I_D = \frac{1}{2} \mu C \left( \frac{w}{L} \right) (V_{gs} - V_t)^2 \\ I_S = I_D + I_{DSS} \quad (\because V_{ds} = V_{gs}) \\ I_D = 1.06 \text{ mA}, V_{ds} = 6.6 \text{ V} \end{cases}$$

$$j_m = \mu C \left( \frac{w}{L} \right) (V_{gs} - V_t) = 0.725 \text{ mA/V}$$

$$R_0 = \frac{V_o}{I_D} = \frac{R_L}{1.06} = 4.75 \text{ k}\Omega$$

$$\begin{cases} I_D = -j_m V_t \left( \frac{1}{R_0} \parallel R_L \right) \\ A_v = \frac{V_o}{V_i} = -3.3 \text{ V/V} \end{cases}$$

Case 2

$$V_i = V_s \times \frac{R_i}{R_{sig} + R_i}$$

$$\frac{V_o}{V_i} = \frac{R_L}{R_i + R_L} = \frac{R_L}{4.75} = 2.33 \text{ mA}$$

$$\frac{V_o}{V_i} = -3.3 \times \frac{R_L}{R_{sig} + R_L}, \text{ if } R_L \gg R_{sig} \Rightarrow \text{no further attenuation}$$


# Consider Voltage Swing (Back to DC)

DC voltage short  
DC voltage open


$$\hat{V}_o = V_{th} = 1.5V \quad \frac{1.5}{3.3} = \hat{V}_i = 0.45V$$

## § 4.7 Single-Stage MOS amplifier

### § The CS amplifier

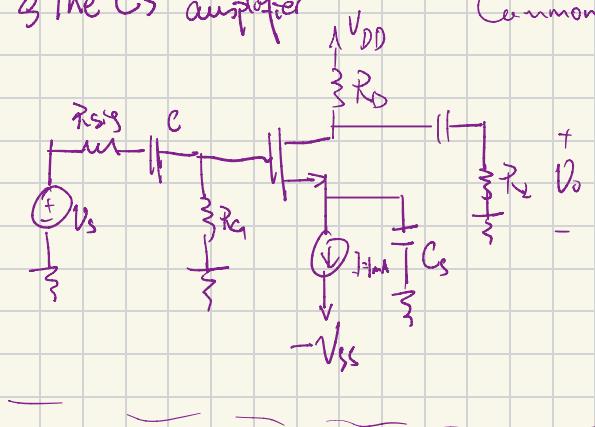

### Common Source

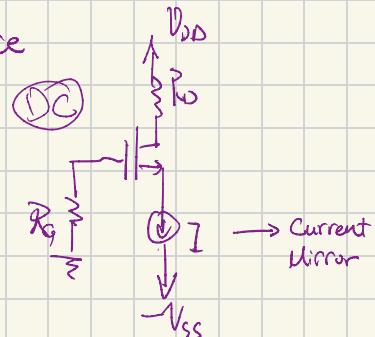

$$I_c \Rightarrow g_m = \sqrt{2\mu C \left(\frac{w}{l}\right) I}$$

Bf Current Source - Mirror:

$$\begin{cases} I_{ref} = \frac{1}{2} \mu C \left(\frac{w}{l}\right) (V_{GS} - V_t)^2 & (1) \\ V_{DD} = I_{ref} R + V_{GS} - V_{SS} & (2) \\ \Rightarrow I_{ref} = Q_1 = Q_2 \Rightarrow I = I_{ref} \end{cases}$$


$$V_D = V_{DD} - IR_D$$

$$I = \frac{1}{2} \mu C \left(\frac{w}{l}\right) (V_{GS} - V_{th})^2$$


$$g_m = \text{ImA/V}$$


(2)

会因之AC/DC

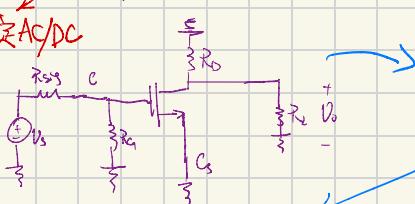

T-model

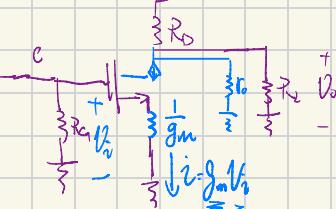


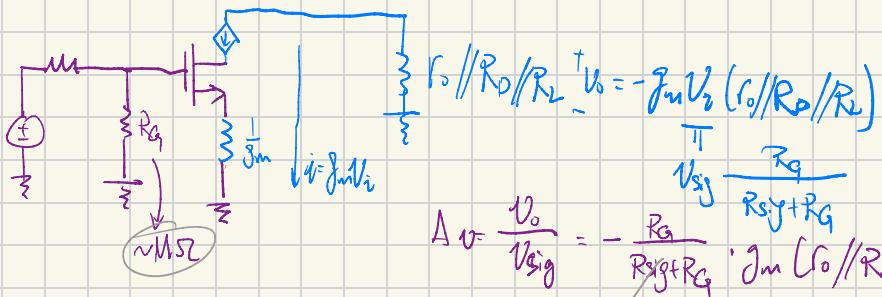


$$A_v = \frac{V_o}{V_{sig}} = -\frac{R_o}{R_{sig} + R_G} \cdot g_m \left( \frac{R_o}{R_o + R_D + R_L} \right)$$

$\downarrow$  Very big


⑦

Consider Early Effect

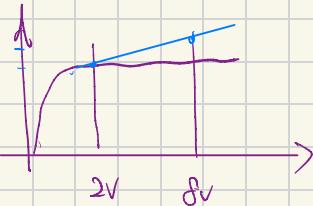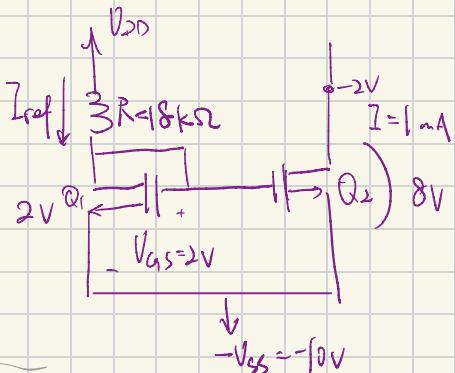

Early Effect:  $I > I_{ref}$


$T_E^2$

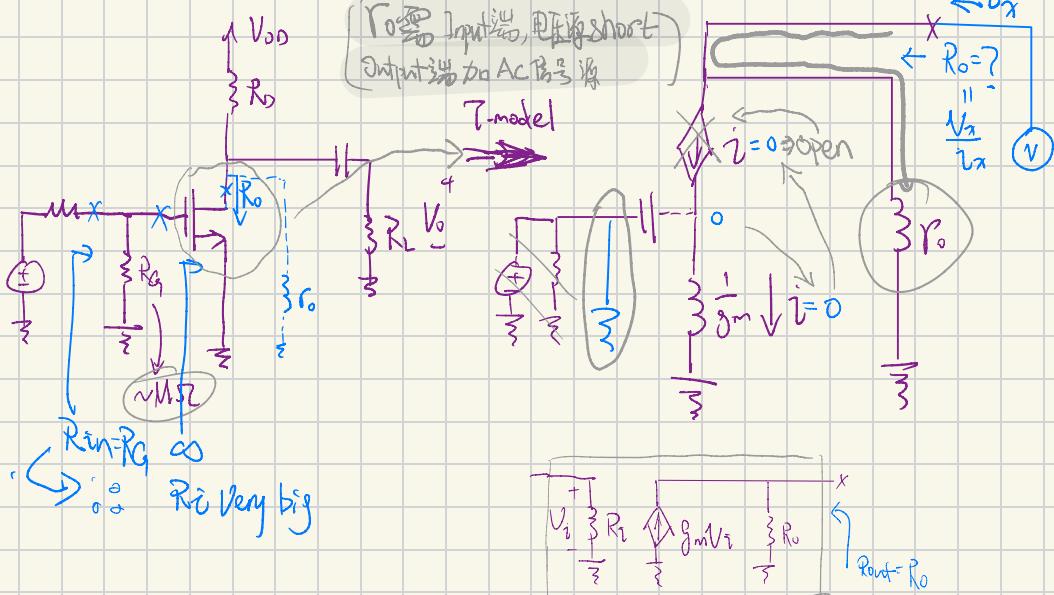

$\left\{ \begin{array}{l} R_i \text{ very large} \\ R_o \text{ very large} \end{array} \right.$

→ close to ideal transconductance amp

↳ reference:

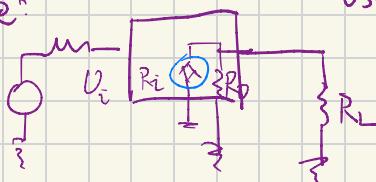

input  
(电压反馈)

$$i_o \approx V_i \cdot g_m$$


所放大信号会  
各种电阻影响

output (电流反馈)

### § 4.7 Single Stage Mos amplifier


### § The CS amplifier with $R_o$

(increases bias stability)

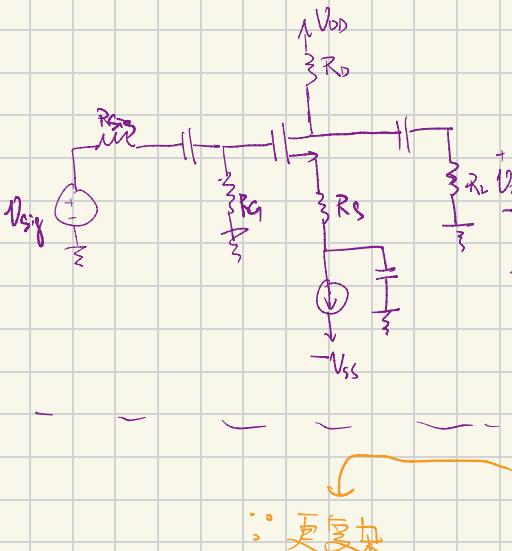

DC similar to above

AC:

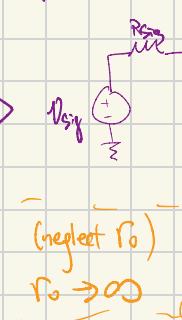

(neglect  $R_o$ )  
 $R_o \rightarrow \infty$

$\therefore$   $R_s, I \downarrow, \text{Gain}$


$$\therefore i_d = \frac{V_o}{R_o + R_s} = \frac{g_m V_i}{R_o + g_m R_s}$$

(current  $i_d$  is reduced  
by a factor of  $1 + g_m R_s$ )



$$\therefore V_o = -i_d (R_o / R_s) = -\frac{g_m}{1 + g_m R_s} V_i (R_o / R_s)$$

$$V_o = \frac{R_o}{R_o + R_s} V_i$$

## § CG (current follower)

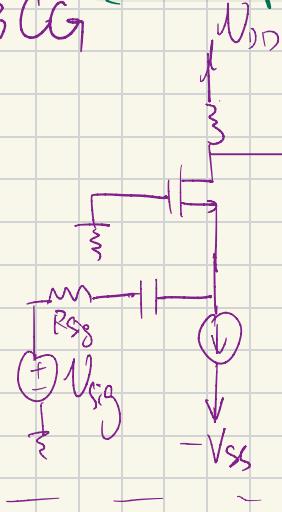

DC: Similar to above

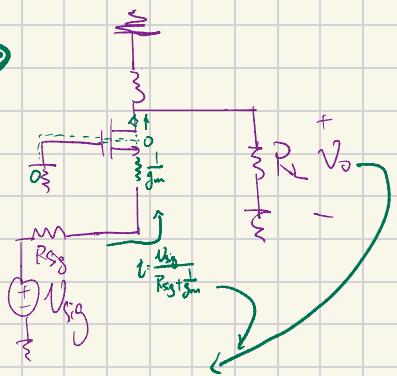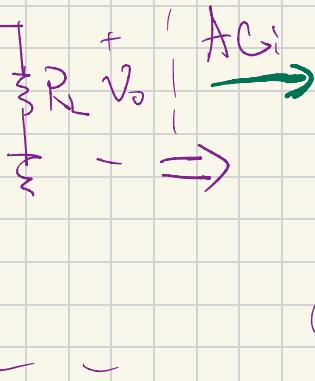

$$CS \quad A_v = \frac{V_o}{V_{sig}} = \frac{g_m (R_D // R_L)}{(1 + g_m R_{sig})}$$

$$V_o = V_{sig} \frac{g_m (R_D // R_L)}{1 + g_m R_{sig}}$$

$A_v$  Reduced by a factor of  $(1 + g_m R_{sig})$   
 $\Rightarrow$  CS gain is largest  $A_v = g_m (R_D // R_L)$

if  $g_m$  is very large  $\Rightarrow g_m R_{sig} \gg 1$ ,


$$V_o = V_{sig} \frac{g_m (R_D // R_L)}{1 + g_m R_{sig}} \Rightarrow \frac{V_o}{V_i} = \frac{R_D // R_L}{R_{sig}}$$

如何理解？



$(R_L/R_D)$

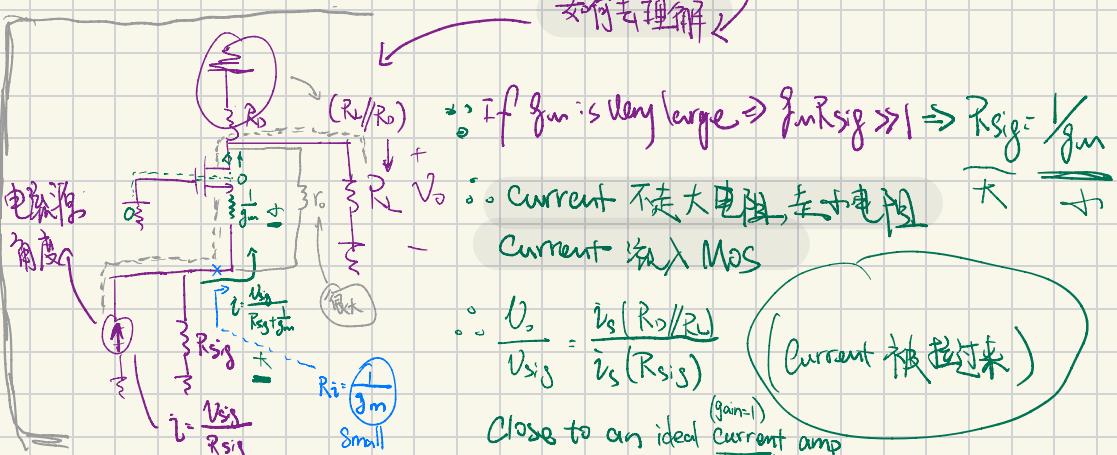$\therefore$  If  $g_m$  is very large  $\Rightarrow g_m R_{sig} \gg 1 \Rightarrow R_{sig} = \frac{1}{g_m}$



$$\therefore \frac{V_o}{V_{sig}} = \frac{V_s (R_D // R_L)}{I_s (R_{sig} + R_BSS)}$$



(Current 被拉过来)

Close to an ideal  $\frac{(gain-1)}{gain}$  current amp

② 8

The CG

○

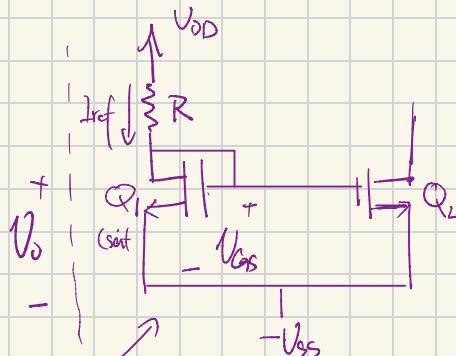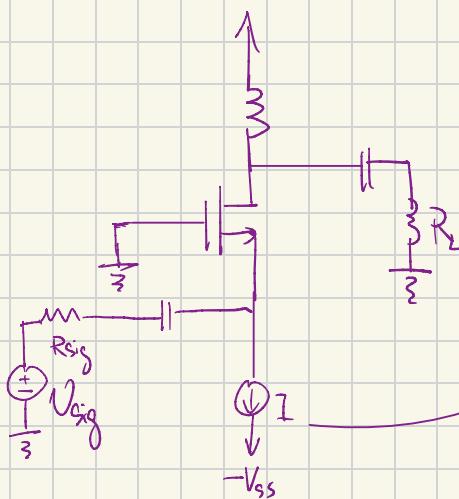



$$\begin{aligned} I_{ref} &= i_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) (V_{DS} - V_{th})^2 \\ I_{ref} &= \frac{V_{DD} - V_{DS} + V_{GS}}{R} \end{aligned}$$

Solve  $I_{ref}, V_{GS}$


Perfect match  $Q_1 = Q_2, I = I_{ref}$

$$g_m = \sqrt{2 \mu C \left( \frac{W}{L} \right) I_D}$$

AC (ignore  $R_f$  now)

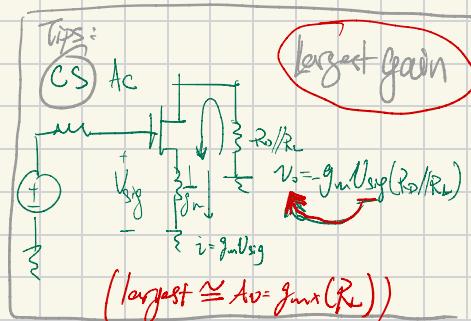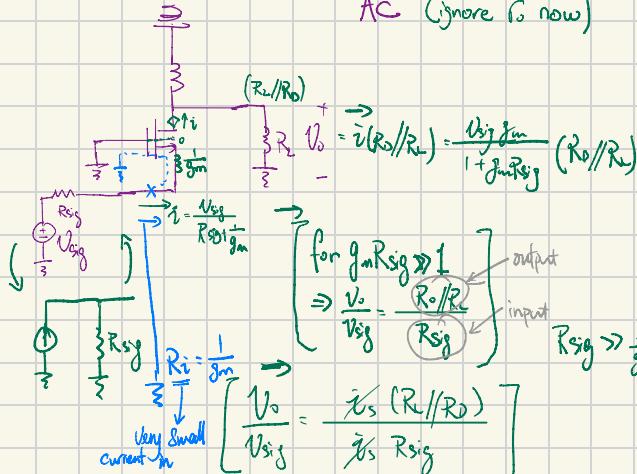

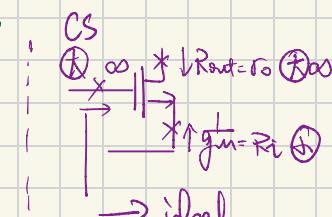
$R_i$  very small  $\Rightarrow$  close to an ideal  
 $R_{out}$  very large  $\Rightarrow$  current amp ( $A_{in}=1$ )



[如果有  $r_o$ , CS largest Gain  $g_m \times (r_o)$  (intrinsic)]


## § CD

(Voltage follower)

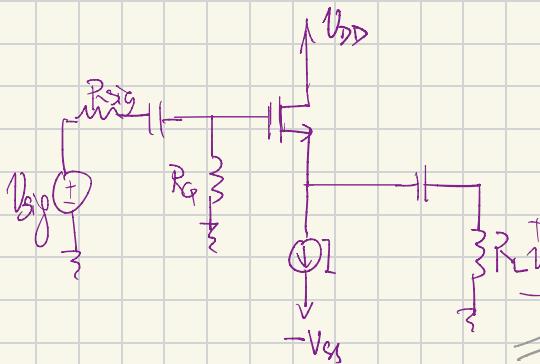

DC similar to above



AC:

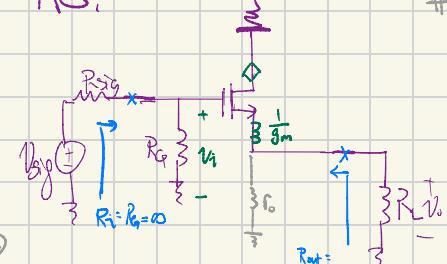

$$\Rightarrow \frac{U_o}{U_{sig}} = \frac{1}{1 + \frac{R_d}{g_m}} \approx 1$$

$\frac{U_{sig}}{U_{sig} + R_g g_m} \approx 1$  very small for  $(r_o \parallel R_d) \gg \frac{1}{g_m}$

(AC  $R_o^2$  short 电极)

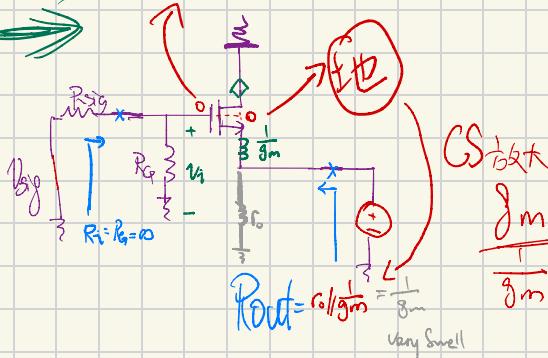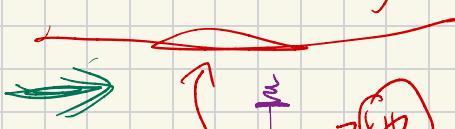

$R_o \rightarrow \infty$   
 $R_o \rightarrow 0$  ideal voltage amp  
 $A_V \rightarrow 1$  ( $\rightarrow$  内电阻无关)




## § 4.8 The MOS internal capacitance and High-f model

$$i_D = \frac{1}{2} \mu C \left( \frac{W}{L} \right) \frac{(V_{GS} - V_t)^2}{V_{GS} + V_{GE}}$$

$$\Rightarrow i_D = g_m V_{GE}$$

indep f  
(linear relation)
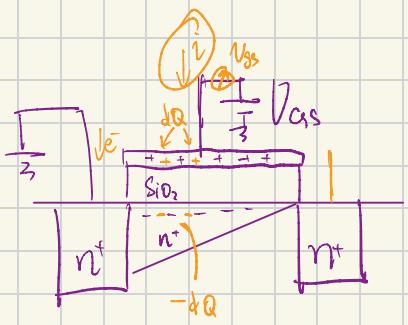
$$O \sin 2\pi f t \quad O \sin 2\pi f t$$



高频率 AC 会有 G 电流

$$dQ = i \frac{dt}{dt} \quad (\text{Time}) \\ = C dV$$

