



(3) BJT:



\downarrow
E-B
Injection

If forward bias,
Injecting electrons
($n \rightarrow P$)

in P,
diffusing
Electrons


in n,
collecting
Electrons

$N_d \gg N_A$

$N_d \gg 1$

$N_A \gg N_D \rightarrow N_D \approx N_A$


$\downarrow N_D = N_A$

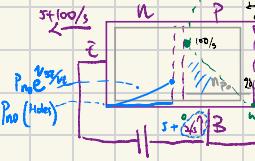

$$V_{BE} \rightarrow (B \frac{1}{2} E_B T_B)$$

In npn, V_{BE} is forward, V_{EB} is reversed

when V_{BE} impose, I_{BS}

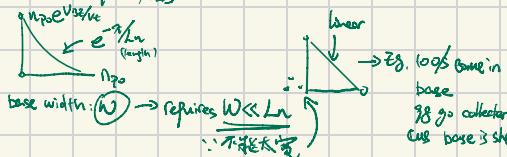

In Active Mode:

$$(B) I_{BS} = \left(\text{To supply the lost holes due to recombination w.r.t. the Injecting electrons} \right) + \left(\text{holes inject from B to E} \right) \rightarrow P_{n0} e^{\frac{V_{BE}}{kT_B}} \cdot \frac{1}{2} \int_{0}^{L_n} D_p \frac{dp}{dx} \Big|_{x=0}$$

$$\left(A_E \frac{1}{2} \times N_p e^{\frac{V_{BE}}{kT_B}} - 1 \right) \cdot w \rightarrow N_p \cdot \frac{w}{L_n} \rightarrow \text{width base} \rightarrow \text{small}$$

\Rightarrow Requirement: $N_p \gg P_{n0}$ ($N_d \gg N_A$)

$$\frac{I_C}{I_S} = f$$

$$\beta = \frac{1}{2} \left(\frac{N_p^2}{D_n L_n} + \frac{D_p}{D_n} \left(\frac{N_A}{N_D} \right) w \right)$$

small small

$$\beta = 100 \quad (\text{gain})$$

Common-Emitter (CE)
Current Gain

Modes of operation

(forward) active
(reverse active)
Cut off
Saturation

E-BJ
Forward
Reverse
forward

Basic: Use of input Voltage to control output current

C-BJ
Forward \rightarrow Amplification
Reverse \rightarrow Reverse (接反了)
forward

$$I_C = A_E Q D_n \frac{dn}{dx} \Big|_w = A_E Q D_n \frac{V_{BE}}{kT_B} \frac{N_A}{N_D} \frac{1}{w}$$

$$I_C = I_S \left(e^{\frac{V_{BE}}{kT_B}} - 1 \right)$$

$\left[V_{BE} \rightarrow \text{charge} \right] \left\{ \text{nonlinear} \right.$
 $\left[V_{BE} \rightarrow \text{small signal} \right] \left\{ \text{linear} \right.$

$$\left(\begin{array}{l} \text{Tips} \\ \frac{dn}{dx} = \int D_n T_n \end{array} \right) \rightarrow \text{lifetime}$$

Active

$$I_C = A_E Q D_n \frac{N_p}{w} \left(e^{\frac{V_{BE}}{kT_B}} - 1 \right)$$

$$\frac{N_p}{N_A}$$

$$\text{CB Common Base}$$


\nearrow Current gain

$$\text{P} \quad \alpha = \frac{i_C}{i_E} \approx 0.99$$

$$I_E = i_C + i_B$$

$$= i_C + \frac{i_C}{\beta} = i_C (1 + \frac{1}{\beta})$$
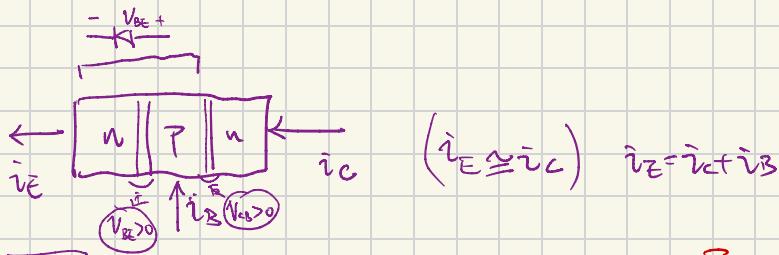
$$\Rightarrow I_C = \frac{\beta}{1+\beta} i_E$$



Active

$$i_E = I_S (e^{V_{BE}/(kT)} - 1), \quad i_C = \frac{i_E}{\alpha} = \left(\frac{I_S}{\alpha}\right) (e^{V_{BE}/(kT)} - 1)$$

Large Signal 模型:



$i_C = \left(\frac{I_S}{\alpha}\right) (e^{V_{BE}/kT} - 1)$ exponential

Tip
Concept: If Active mode β_R ,
则不理想, 因为 $\beta_R \neq \beta$ $\rightarrow \alpha \approx 0.1$
 $\beta = \frac{\alpha}{1-\alpha} \approx 0.1$ (β_R)
Prove:
Planar

β_R $\beta_R = \frac{i_C}{i_B}$

(36)

Active mode:

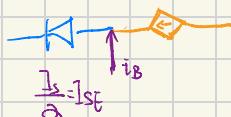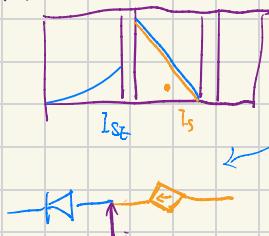

$i_C = 2i_E$

$\alpha \approx 8.99$

$$i_C = A_E q D_n \frac{n_p}{W} (e^{V_{BE}/kT} - 1) + A_E q D_p \frac{P_{Lp}}{W} (e^{V_{BE}/kT} - 1)$$
 $= (A_E q D_n \frac{n_p}{W} + A_E q D_p \frac{P_{Lp}}{W}) (e^{V_{BE}/kT} - 1)$


i_{SE}

$$i_C = A_E q D_n \frac{n_p}{W} (e^{V_{BE}/kT} - 1) - A_E q \frac{1}{W} n_p (e^{V_{BE}/kT} - 1)$$


$I_S \downarrow 100/S$

\therefore 为了简单, 忽略基区的失效率 $\downarrow 2/S$ lost hole


Reverse Active mode:

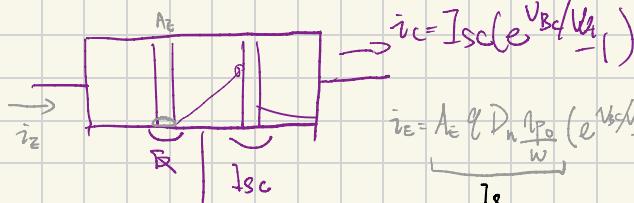

model:

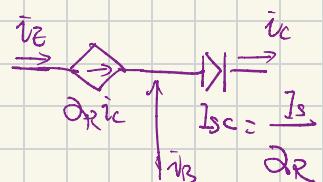


Saturation

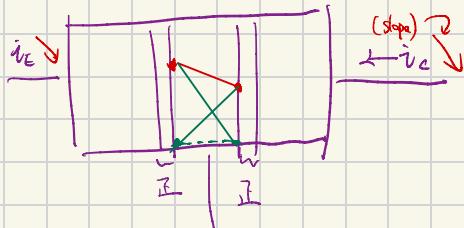

Ebers-Moll Model

可換式線性模型: $N(V_{BE}, V_{BC}) = N(V_{BE,0}) + N(0, V_{BC})$

	Forward	Reverse Active
i_{CE}	$\frac{I_s}{\alpha_F} e^{V_{BE}/V_{T_F}} - I_s$	$\frac{I_s}{\alpha_R} e^{-V_{BC}/V_{T_R}} - I_s$
i_{CB}	$\frac{I_s}{\alpha_F} e^{V_{BC}/V_{T_F}} - I_s$	$\frac{I_s}{\alpha_R} e^{-V_{BE}/V_{T_R}} - I_s$

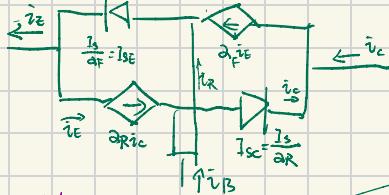

正, 反都用

Saturation

所有节点都
可描述

Linear Matrix

$$i_E = \frac{I_s}{\alpha_F} \left(e^{\frac{V_{BE}}{V_T} - 1} \right) - \frac{I_s}{\alpha_R} \left(e^{\frac{V_{BC}}{V_T} - 1} \right)$$

$$i_C = I_s \left(e^{\frac{V_{BE}}{V_T} - 1} \right) + \frac{I_s}{\alpha_R} \left(e^{\frac{V_{BC}}{V_T} - 1} \right) \quad \text{reverse leakage current}$$


$$i_B = \frac{I_s}{\alpha_F} \left(e^{\frac{V_{BC}}{V_T} - 1} \right) + I_s$$

$$i_E = \frac{I_s}{\alpha_F} \left(e^{\frac{V_{BE}}{V_T} - 1} \right) - \alpha_R \frac{I_s}{\alpha_R} \left(e^{\frac{V_{BC}}{V_T} - 1} \right)$$




$$i_B = i_E - i_C$$

$$\frac{I_s}{\alpha_R} \left(e^{\frac{V_{BC}}{V_T} - 1} \right) + \frac{I_s}{\alpha_F} \left(e^{\frac{V_{BC}}{V_T} - 1} \right)$$


(37)

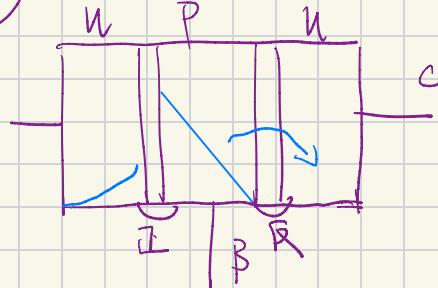


Active:

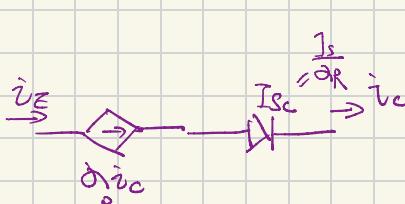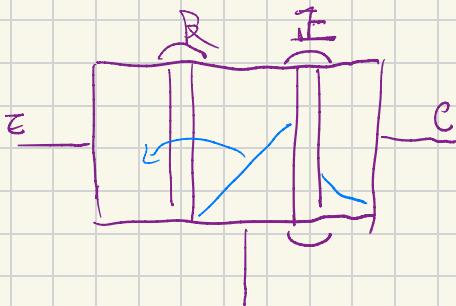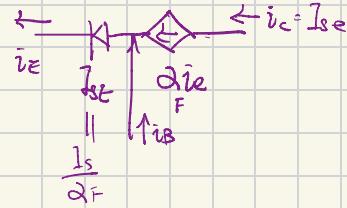

§ circuit symbol

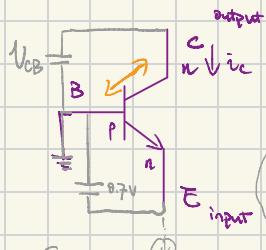

C-B output characteristic

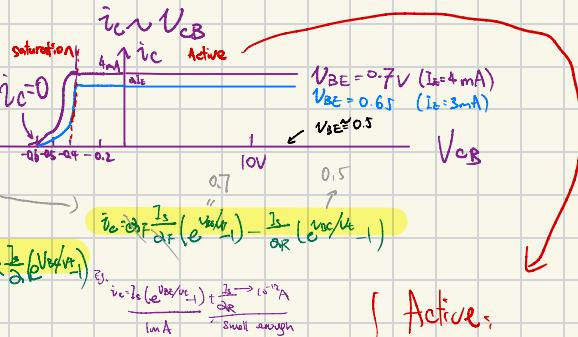

A p-n junction does not become effectively forward biased until the voltage exceeds $\approx 0.4V$

Active:


E-B Junction

$$V_{BE} = 0.6 \text{ to } 0.8V$$

C-B Junction

$$\approx 0.7V$$

(forward)

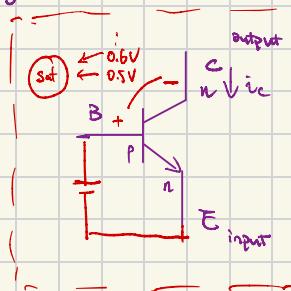

Saturation

$$\text{forward} \\ V_{BE} = 0.7V$$

Reverse forward

$$V_{BE} < 0.5V$$

反向正向不導通

forward ($> 0.5V$)

§ Ebers - Moll Model

Eg. If the transistor has $\beta = 100$ and a $V_{BE} = 0.7V$ at $i_C = 1mA$

Design the circuit so that $i_C = 2mA$ & $V_C = 5V$

\rightarrow find I_S

(? mode)

$$\text{① } i_C \approx I_S (e^{V_{BE}/V_T})$$



$$\text{② } (SOL) i_C = I_S e^{V_{BE}/V_T}$$

\therefore Active

$$\beta = \frac{I_C}{I_S} \quad 2 = \frac{I_C}{I_S}$$

$$I_C = I_S + I_B$$

$$0.5 = I_S$$

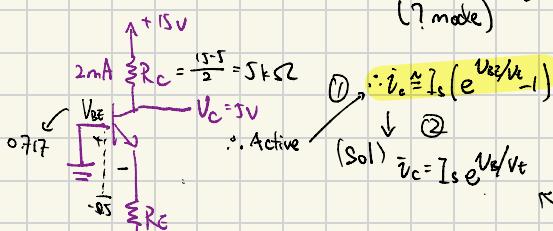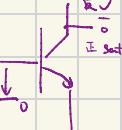

$$R_E = \frac{-0.717 + 15}{2.02} = 7.07k\Omega$$


$$\text{⑧ } I_E = \frac{I_C}{\beta}$$

$$= 2.02mA$$

Assume $V_{BE} = 0.7 \text{ V}$, \rightarrow get 7.079

\Rightarrow 呈現 active 狀態 ≈ 0.7
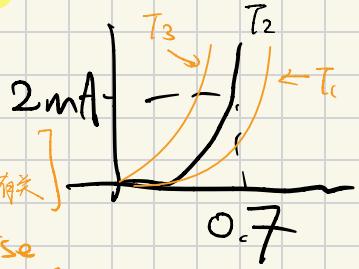
$$\begin{bmatrix} T_3 > T_2 > T_1 \\ T \rightarrow I_s \uparrow \end{bmatrix} \quad \begin{bmatrix} I_s(T) \\ I_s \propto T^{\alpha} \end{bmatrix}$$




$$AV_{BE} = -2 \text{ mV/}^{\circ}\text{C rise}$$

(con)

$$I_s(T) \uparrow$$

$\Rightarrow \alpha, \beta$
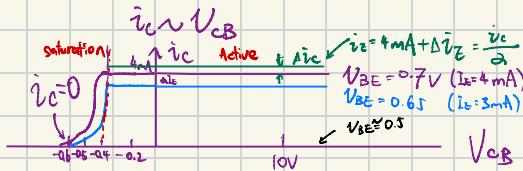
$$\alpha = \frac{i_c}{V_E} \quad \text{total (large signal)}$$





$$\alpha_{ac} = \frac{\Delta i_c}{\Delta V_{BE}} \quad (\alpha = \alpha_{ac})$$

↳ Small Signal

$$\beta_{ac} = \left| \frac{\Delta i_c}{\Delta i_B} \right| \text{ at } V_{CE} = \beta$$

§ CE output characteristics

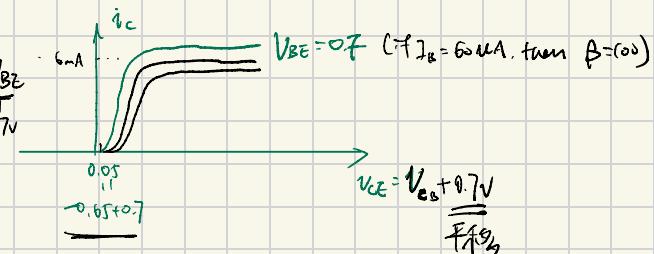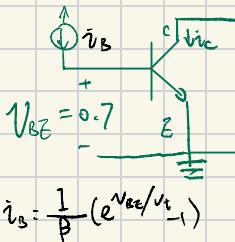

28



§ The CE output characteristic


Eber-Moll equations

$$i_C = I_s (e^{V_{BE}/V_t} - 1) - \frac{I_s}{\alpha R} (e^{V_{CE}/V_t} - 1)$$

$$i_E = \frac{I_s}{\alpha} (e^{V_{BE}/V_t} - 1) - I_s (e^{V_{CE}/V_t} - 1)$$
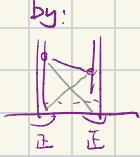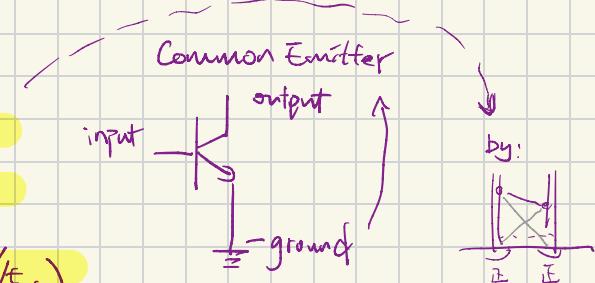
$$i_B = \frac{I_s}{\alpha} (e^{V_{BE}/V_t} - 1) + \frac{I_s}{\alpha R} (e^{V_{CE}/V_t} - 1)$$



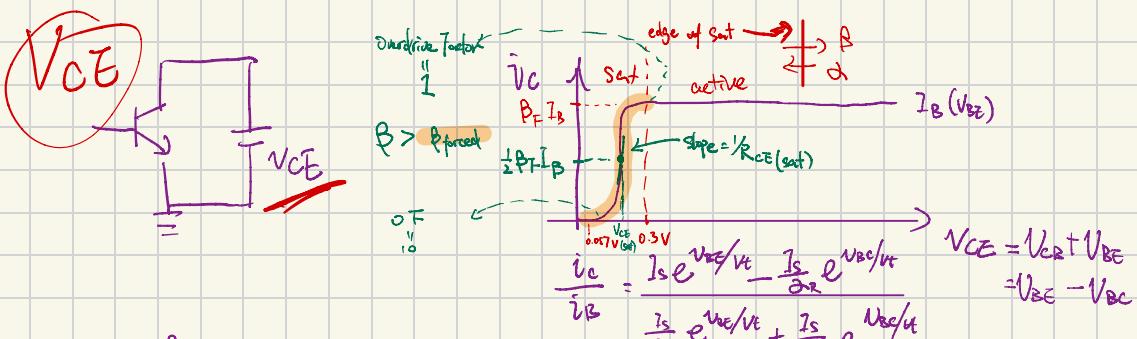

→ for $i_c = 0$

$$V_{CE} = V_t \ln \left(\frac{1}{\beta R} \right) = 0.057V$$

→ for a large V_{CE}

$$\underline{i_c = I_B \beta_F}$$

$$\beta_R = \frac{\beta R}{1-\beta R} = \frac{0.1}{0.9} = 0.11, \quad \beta_F = 100, \quad e^{\frac{V_{CE}}{V_t}} \gg \frac{\beta_F}{\beta_R} = 1000$$


$$V_{CE}(\text{EoS}) = 0.3V$$

$$0.057V \xrightarrow{\text{Sat}} 0.3V$$

$$\frac{1}{2} \beta_F = \frac{e^{\frac{V_{CE}}{V_t}} - \frac{1}{\beta_R}}{\frac{1}{\beta_F} e^{\frac{V_{CE}}{V_t}} + \frac{1}{\beta_R}} \Rightarrow \frac{1}{2} + \frac{\beta_F}{\beta_R} = e^{\frac{V_{CE}}{V_t}} \Rightarrow \underbrace{V_{CE}}_{(\text{Sat})} = V_t \ln \left(\frac{\beta_F}{\beta_R} + \frac{2}{\beta_R} \right) = V_t \ln \left(\frac{100}{0.11} + \frac{2}{0.11} \right) = 0.173V$$

$$\boxed{\text{If } V_{CE} \rightarrow \text{sat}, \quad V_{CE}(\text{sat}) = 0.2V}$$

Sat.

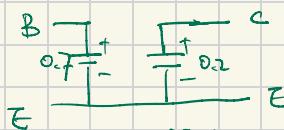

$$(Sat) \quad I_c(\text{sat}) < \beta I_B$$

$$\left[\beta_{\text{forced}} = \frac{I_c(\text{sat})}{I_B} < \beta \Rightarrow \frac{\beta}{\beta_{\text{forced}}} \equiv \text{overdrive factor} \right]$$


The greater the overdrive factor the deeper the transistor is driven into sat.

Early Effect CB

Eg.



→ implement 3 equations.

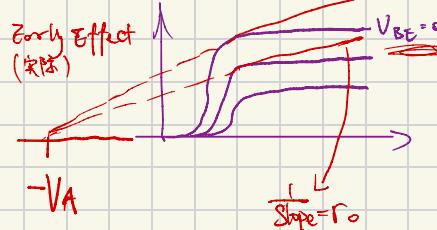

$$V_{CE} = V_{CE0} + V_{BE}$$

collector Junction depletion width widen



$$I_c = I_{SO} \frac{V_{CE}}{V_A} \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$I_c = I_S \left(e^{\frac{V_{BE}}{V_T}} \right)$$

$$I_S = A_e q D_n \frac{n_p}{w} e^{\frac{V_{BE}}{V_T}}$$

$$\frac{1}{w - \Delta w} = \frac{1}{w(1 - \frac{\Delta w}{w})} \approx \frac{1}{w} \left(\frac{\Delta w}{w} \right)$$

$$\left(\frac{\partial I_c}{\partial V_{CE}} \right) = r_o$$

余上不去
for a const 1/V_T

$$\left(\frac{I_c}{V_A} \right)^{-1} = \boxed{\frac{V_A}{I_c}}$$


$$\Delta w \propto V_{CE} \Rightarrow \Delta w = \lambda' V_{CE}$$

(linear \approx)

$$\frac{1}{V_A}$$

(39)

§ CE Common Emitter

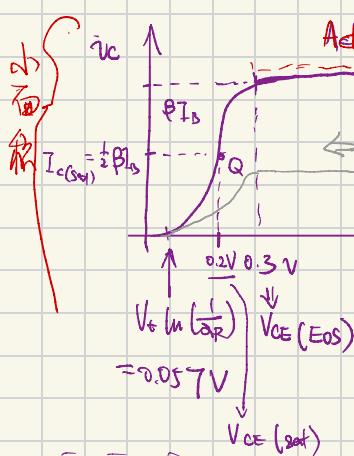

$$\text{Active } \beta \equiv \frac{I_c}{I_B}$$

$$\alpha = \frac{\alpha}{\alpha + 1}$$

$$\alpha_R = 0.1$$

$$\beta_F = 0.99 \Rightarrow$$

$$\boxed{V_{CE} > V_{CE(\text{sat})}, I_c(\text{sat}) < \beta I_B}$$

$$\boxed{\beta_{\text{forward}} = \frac{I_c(\text{sat})}{I_B} < \beta}$$

The transistor is forced in "Sat"


$$\begin{aligned} I_B &= \frac{I_c}{\beta} \\ I_c &= \alpha I_E \\ \alpha &= \frac{\beta}{\beta + 1} \end{aligned}$$

$$\begin{aligned} V_{CE(\text{sat})} &= 0.3 \text{ V} \\ V_{CE} &+ V_{CE(\text{sat})} > 0.3 \text{ V} \end{aligned}$$


for active, $V_{CE} > 0.3$

$$V_{CB} + V_{BE} > 0.3 \Rightarrow V_{CB} > -0.4 \Rightarrow V_C - V_B > -0.4 \Rightarrow V_C > V_B - 0.4$$


§ PnP transistor

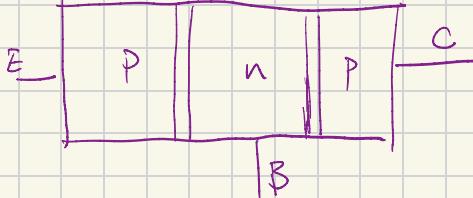


Active

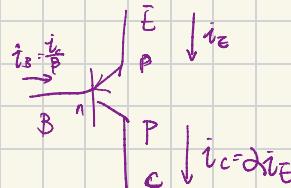

PnP / Amplifier

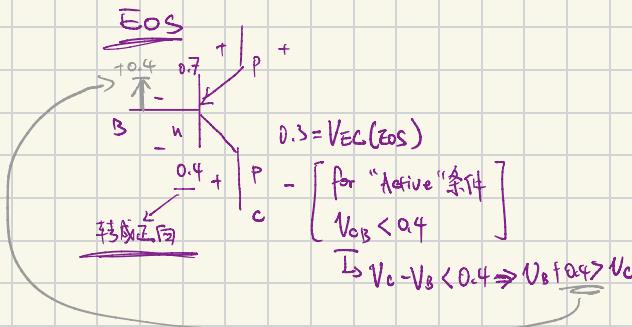

§ The BJT as an amplifier - as a switch

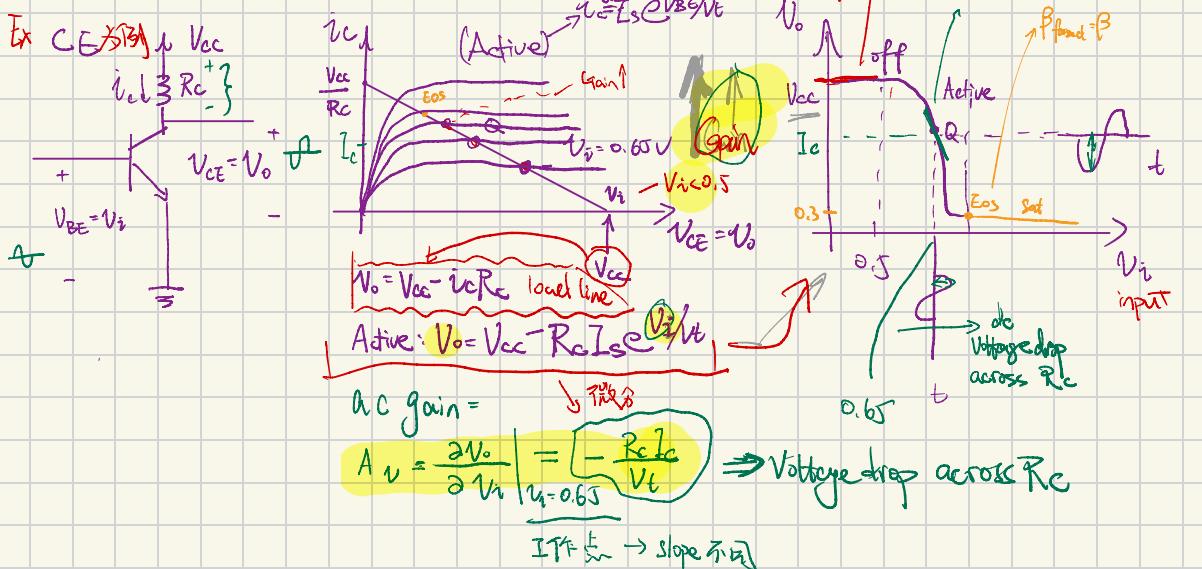


§ 5.2

A CE current using a BJT having $I_S = 10^{-15} \text{ A}$, $R_C = 6.8 \text{ k}\Omega$, $V_{CC} = 10 \text{ V}$

第 5 章

BJT
0.7 V_{BE}

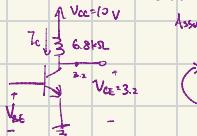a) $V_{CE} = ?$ for $V_{BE} = 3.2 \text{ V}$




Assume "Active"

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \Rightarrow V_{BE} = 6.908 \text{ mV} \Rightarrow 0.69 < 3.2 \text{ Active.} \\ I_C = \frac{10 - 3.2}{6.8} = 1 \text{ mA}$$

b) at this p+ $\rightarrow A_{11} = \frac{10 - 3.2}{V_T} = -272 \text{ V}_1$

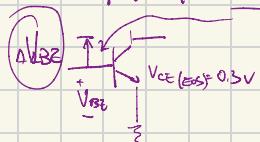
c) find the positive increment in V_{BE} that drives the BJT to EOS



$$I_C(EOS) = \frac{10 - 0.3}{6.8} = 1.617 \text{ mA}$$

$$\Delta V_{BE} = V_T \ln \frac{I_C}{I_C(EOS)} = V_T \ln \frac{1.617 \text{ mA}}{1 \text{ mA}} = 12 \text{ mV} \\ \approx 0.7 \text{ V}$$

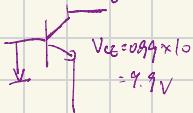d) find the negative increment in V_{BE} that drives BJT to within 1% of cut off (ie. $I_C = 0.99 I_{C(EOS)}$)




$$I_C = \frac{10 - 0.99}{6.8} = 0.0147 \text{ mA}$$

$$\Delta V_{BE} = V_T \ln \frac{0.0147 \text{ mA}}{1 \text{ mA}} = -10.5 \text{ mV}$$

1% cut off

$$V_{BE} - \Delta V_{BE} = 6.908 \text{ mV} - 0.5 \text{ mV} \approx 590 \text{ mV}$$

Practical

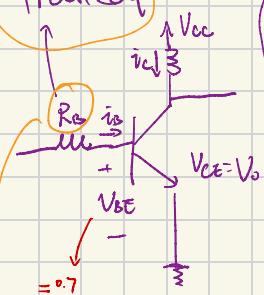

近似

$$i_B = \frac{i_C}{\beta} = \frac{i_S (e^{V_{BE}/V_T})}{\beta} \Rightarrow i_B \propto V_{BE} \text{ (exponential law)}$$




load line
 $i_B = i_S R_L + V_{BE}$

slope ≈ 0.7

$$\text{think as ideal} \rightarrow i_B = \frac{V_{BE} - 0.7}{R_B}$$

$V_{BE} = 0.7$
linear $\neq i_B$

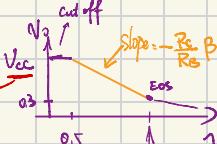

Assume "Active" $i_C = \beta i_B$

$$V_{BE} = V_{CC} - i_C R_C = V_{CC} - \beta \frac{V_{BE} - 0.7}{R_B} R_C$$

$$\left(0.7 + i_B (R_C - R_B) \right) = 0.7 + \frac{R_B (V_{BE} - 0.7)}{R_C}$$

$$I_C(EOS) = \frac{V_{CC} - 0.3}{R_C} \Rightarrow I_B(EOS) = \frac{I_C(EOS)}{\beta}$$


$\beta \approx 100$

Slope! AC 信号
放大倍数

放大倍数

Saturation

as a switch $V_{in} = V_{cc}$ or 0

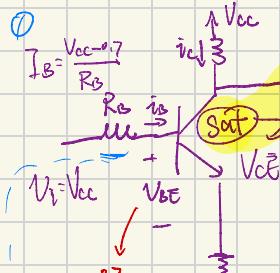


$$I_B = \frac{V_{cc} - 0.7}{R_B}$$

$$I_C(\text{sat}) = \frac{V_{cc} - 0.2}{R_C}$$

$$\beta_{\text{forced}} = \frac{I_C(\text{sat})}{I_B} = \frac{\frac{V_{cc} - 0.2}{R_C}}{\frac{V_{cc} - 0.7}{R_B}} \approx \frac{R_B}{R_C}$$

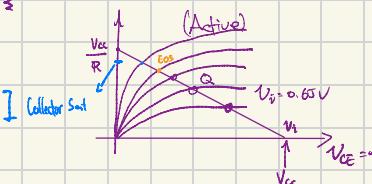The deeper the BJT is
The smaller the β_{forced} is




β = Working
 β_{forced}

$$\beta_{\text{forced}} = \frac{i_c(\text{sat})}{i_B}$$

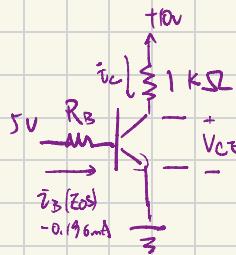(4)

Ex 5.3 β in the range of 50 to 500

find R_B that results in sat, with an overdrive factor of at least 10



(EOS)

$$i_C(\text{EOS}) = \frac{0.2}{1k\Omega} = 0.2 \text{ mA}$$


$$i_B(\text{EOS}) = \frac{i_C(\text{EOS})}{\beta} = \frac{0.2}{50} = 0.004 \text{ mA}$$

Set I_B to $i_B(\text{EOS})$

~~β~~

so to saturate

找最小的要 worst case 也 sat

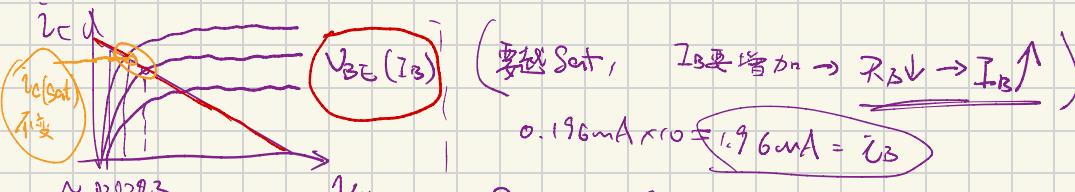


$$0.196 \text{ mA} \times 10 = 1.96 \text{ mA} = i_B$$

$$\beta_{\text{forced}} = \frac{9.8}{1.96} = 5$$

$$\frac{\beta}{\beta_{\text{forced}}} = \frac{50}{5} = 10$$

Ex 5.4

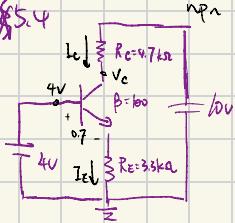

Find all node voltages & branch currents

(sol) Assume "Active"

$$I_E = \frac{4 - 0.7}{3.3} = 1 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{1 + \beta} I_E = 0.99 \text{ mA}$$


$$V_C = 10 - I_C R_C = 10 - 0.99 \times 4.7 = 5.3 \text{ V}$$

$\beta > 4 \rightarrow \text{Reverse} \rightarrow \text{Active}$


$$I_B = \frac{I_E}{\beta} = \frac{0.99}{100}$$

Tips: if $V_C < V_E$ reverse

(btw) $V_C > 4V - 0.5V$

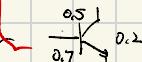

Ex 5.5

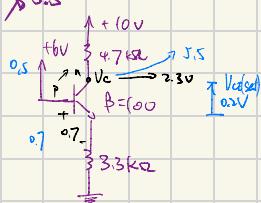

Assume "Active"

$$I_E = \frac{6 - 0.7}{3.3} = 1.6 \text{ mA}$$

$$I_C = \alpha I_E = 1.58 \text{ mA}$$

$$V_C = 10 - 1.58 \times 4.7 = 2.5 \text{ V}$$

$$\left. \begin{array}{l} 6V - 0.5V = 5.5 \\ 5.5 > 2.5 \end{array} \right\} \text{not "Active"}$$

Saturation:

$$V_C = 6 - 0.5 = 5.5$$

$$I_C = \frac{10 - 5.5}{4.7 k\Omega} = 0.16 \text{ mA}$$


$$I_E = 1.6 \text{ mA}$$

$$I_B \times \frac{I_C}{\beta}$$

$$I_B = I_E - I_C = 1.6 - 0.16 = 0.64 \text{ mA}$$

$$I_{B,\text{forced}} = \frac{0.64}{0.64} = 1.5 \quad \beta = 100$$

Ex 5.6

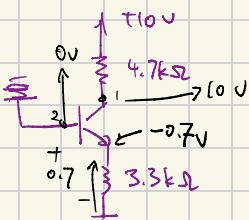


Assume "Active"

$\because V_B < V_E \therefore$ current goes node $-0.7V$ not "Active"

Cut off

node 1 = 0 node 2 = 0 all current = 0

Ex 5.7

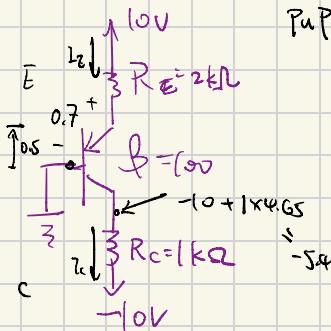


Assume "Active"

$$I_E = \frac{10 - 0.7}{2} = 4.65 \text{ mA}$$

$$I_C = \beta I_E \approx 4.65 \text{ mA}$$

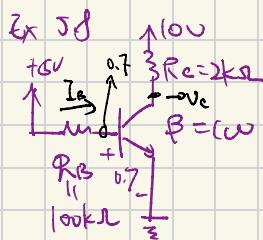
$\because 0 + 0.7 > -5 \text{ V} \rightarrow \text{Reverse}$



$1.4 > 0.7 \rightarrow \text{Reverse} \rightarrow \text{Active}$

$$1.4 - 0.7 = 0.9 > 0.7$$

Ex 5.9

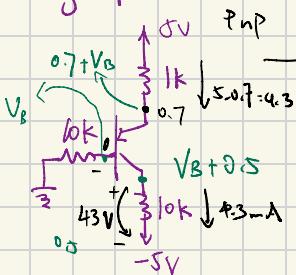

$$I_E = \frac{10 - (V_B + 0.7)}{1} \rightarrow \text{Solve } V_B = 3.13$$


$$I_C = \frac{V_B + 0.7 + I}{10} + \frac{V_B}{10} \rightarrow I_C = 0.36 \text{ mA}$$

$$I_B = 0.36 \text{ mA}$$


$$I_E = I_C + I_B$$

$$\beta_{\text{found}} = \frac{0.36}{0.31} = 2.8 < \beta$$

5.10

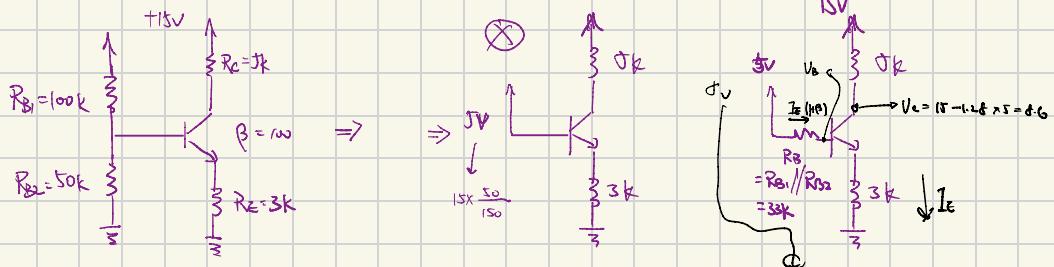

5.11

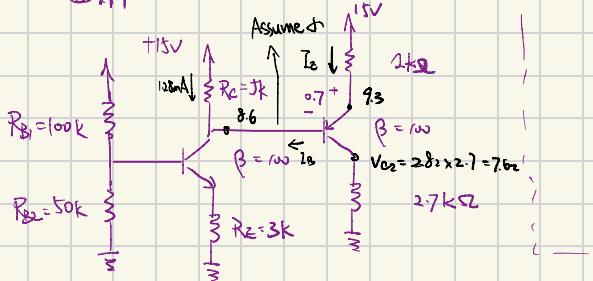

Assume 'active'

$$I = \frac{I_C}{1+\beta} \times 33 + 0.7 + I_C \cdot 3$$

$$\Rightarrow I_C = 1.28mA \Rightarrow I_C = 1.28mA$$

$$V_{CE} = 15 - 1.28 \times 3 = 8.6V$$

$$V_B = 1.28 \times 3 + 0.7 = 4.57V$$

$8.6V > 4.57V \rightarrow \text{NPN} \rightarrow \text{Active}$

18.4.1


Transistor effect

Assume $I_B \ll I_C \rightarrow$ Assume $I_B \ll I_C$

$$\left\{ \begin{array}{l} I_C = \frac{15 - V_B}{2k} = 2.85mA \\ I_C = \beta I_B = 2.85mA \end{array} \right.$$

$$\left\{ \begin{array}{l} I_B = \frac{I_C}{\beta} = 0.0285mA \\ \text{Assume } I_B \ll I_C \end{array} \right.$$

5.12

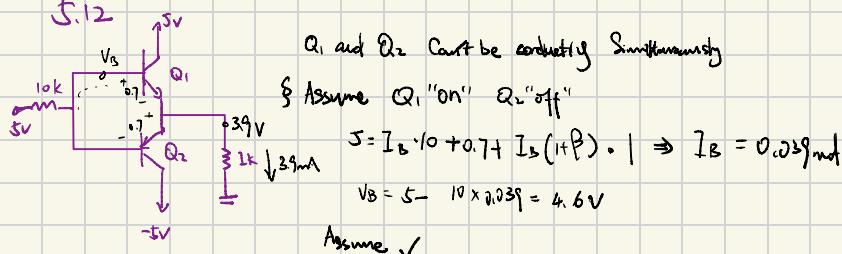

Q_1 and Q_2 Can't be conducting Simultaneously

Assume Q_1 "on" Q_2 "off"

$$I = I_B \cdot 10 + 0.7 + I_D(1+\beta) \cdot 1 \Rightarrow I_B = 0.039mA$$

$$V_B = 5 - 10 \times 0.039 = 4.6V$$

Assume ✓

$$I_C = \frac{\beta}{1+\beta} I_E$$



$$I_C = \beta I_E = \frac{1}{1+\beta} I_E$$

$$I_B = I_E(1+\beta)$$

41

§ 5.5 Biasing in BJT amplifier circuit

Biasing (拉回來)

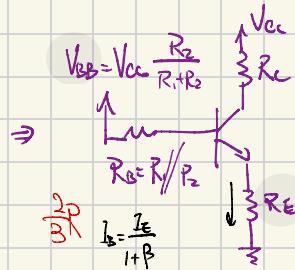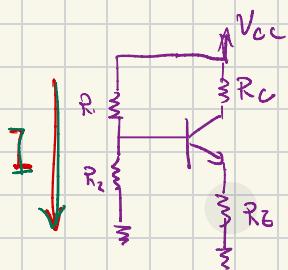

$$\frac{I_c}{1+\beta}$$

$$V_{bb} = I_b R_b + V_{be} + I_c R_c$$

$$I_b = \frac{V_{bb} - V_{be}}{R_b + \frac{R_c}{1+\beta}}$$

V_{be} & β \Rightarrow BJT 有关

$$\Delta I_c = \frac{\partial I_c}{\partial V_{bb}} \Delta V_{bb} + \frac{\partial I_c}{\partial \beta} \Delta \beta$$

越小 ΔI_c 越大 ΔV_{bb} $\Delta \beta$
dc stability ↑

Tips:

($\uparrow V_{bb} \Rightarrow I_b \uparrow, I_c \uparrow, I_e \uparrow$)
 \Rightarrow push BJT into saturation
 $\downarrow I_b \downarrow$ \Rightarrow $I_c \downarrow$ \Rightarrow $R_E \gg \frac{R_C}{1+\beta}$
 $V_{bb} > V_{be}$

$$\Rightarrow I_c = \frac{V_{bb}}{R_E} \quad \text{influence of BJT}$$

电容耦合

$\therefore V_{bb}$ 不能太大

Rule of thumb for Design

$$\left\{ \begin{array}{l} 0. I_c R_c \approx \frac{1}{3} V_{cc} \\ 0. V_{ce} \approx \frac{1}{3} V_{cc} \\ 0. V_{bb} \approx \frac{1}{3} V_{cc} \\ 0. I = \alpha I_c \approx I_c \end{array} \right.$$

$\frac{1}{3}$ 压降
 $\frac{1}{3}$ 压降
 $\frac{1}{3}$ 压降
 $\frac{1}{3}$ 压降
 $\frac{1}{3}$ 压降

$$R_E \gg \frac{R_C}{1+\beta} \rightarrow R_E \text{ 在 } 1/3 \text{ 段时可决定, 小要决定 } R_B \leftarrow$$


$$\frac{1/3 V_{cc}}{I_E} \gg \frac{R_C / 2R}{\beta} \Rightarrow I_E \ll \beta I \Rightarrow I \gg \frac{I_E}{\beta}$$

偏压稳定性
 $\left(\text{to avoid the attenuation of the input signal} \right)$
the smaller I_b the better


$$\left(\text{neglect } I_B \Rightarrow V_{cc} \times \frac{R_2}{R_1 + R_2} = \frac{1}{3} V_{cc} \Rightarrow R_1 = 2R_2 \right)$$

$$I \gg 0.01 I_c$$

$$I = 0.1 I_c \text{ or } I_c$$

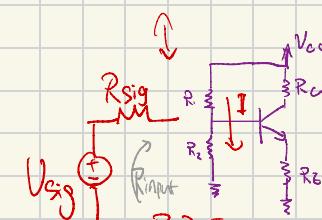

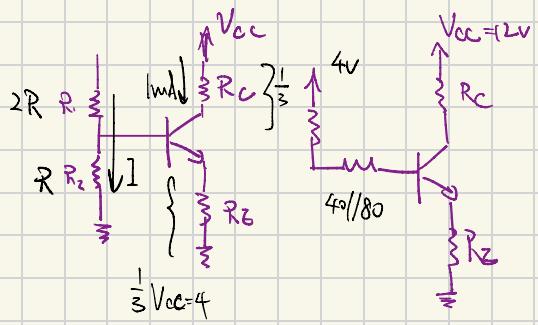R_1, R_2 需够大
才能让分压进入电路
 $(I \downarrow, R \uparrow)$



Design to have $I_E = 1mA$
for $V_{cc} = 12V$, $\beta = 100$

Bias by R_E ,
 V_{BB} , R_B

$$(so) R_C = \frac{4}{1} = 4k\Omega$$

$$R_E = \frac{4-0.7}{1mA} = 3.3k\Omega$$

[neglect I_B :

$$4 = \frac{R_E}{R_E + R_C} \cdot 12, I = \frac{1}{3R} = 0.1I_E \Rightarrow R = 40k\Omega$$

Let $I = 0.1I_E$ ($I = 1$, $I_E = 4k, 8k$)

Consider $I_B \neq 0$



$$I_E = \frac{4-0.7}{3.3k + \frac{40}{1+100}} = 0.95mA$$

$\downarrow g_o 3k$ $\rightarrow 1mA$

电流放算

(P2) 偏压电路

Biasing in BJT amplifier

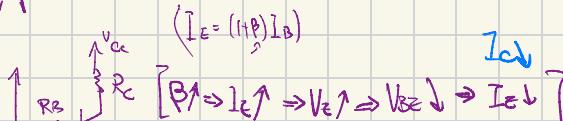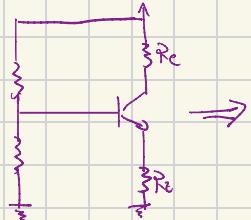

$$(I_E = (1+\beta)I_B)$$


I_{CB}

$\beta \uparrow \Rightarrow I_E \uparrow \Rightarrow V_E \uparrow \Rightarrow V_{CE} \downarrow \Rightarrow I_E \downarrow$


提供dc
偏压稳定性

偏压稳定性

$$I_E = \frac{V_{BE}}{R_E}$$

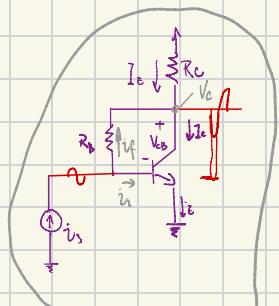

δ

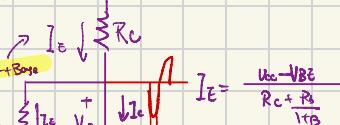

$$I_E = \frac{V_{cc} - V_{BE}}{R_E + R_B + \frac{1}{\beta}}$$

V_{BE}, β dep on BJT

$$\text{If } R_E \gg R_B \Rightarrow I_E = \frac{V_{cc}}{R_E} \text{ indep of BJT}$$



R_B 不能太小 $\therefore V_{BE} \downarrow = I_B R_B \downarrow \Rightarrow$ output voltage swing \downarrow

$$\beta \uparrow \Rightarrow I_E \uparrow (I_E \downarrow) \Rightarrow V_{CE} \downarrow \Rightarrow i_i \downarrow \Rightarrow I_E \downarrow$$

(if \uparrow)

(Tips: R_B 不能过大或过小)

§ Biasing Using a current Source

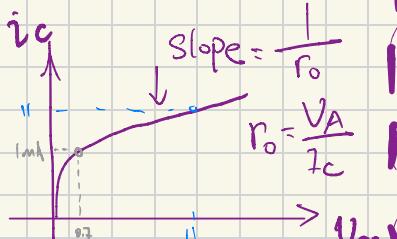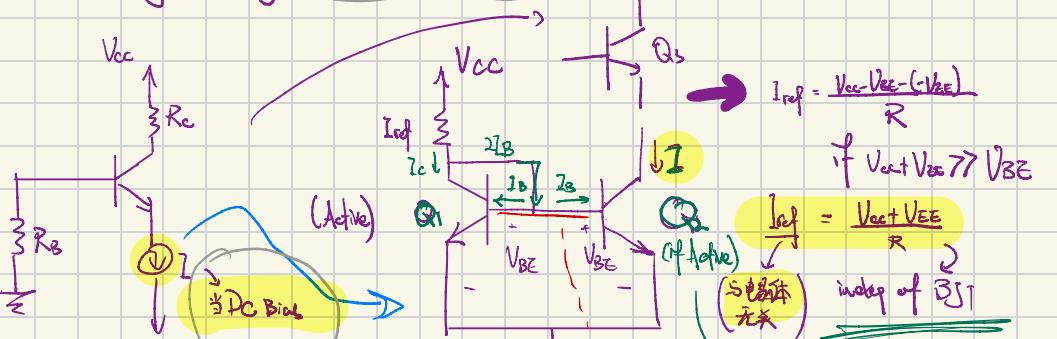


电晶体一定会有关 Early Effect

$$\because I_{ref} = I_c + 2I_B \quad \text{①}$$

$$= \frac{I_c + 2\frac{I_c}{\beta}}{\beta} \Rightarrow I_c \left(1 + \frac{2}{\beta}\right) = I_c \quad \text{②} \Rightarrow I_c = I_c$$

$\because V_{BE}$ 相等 (Q_1 & Q_2), β 一样 $\therefore I_c$ 就会一样
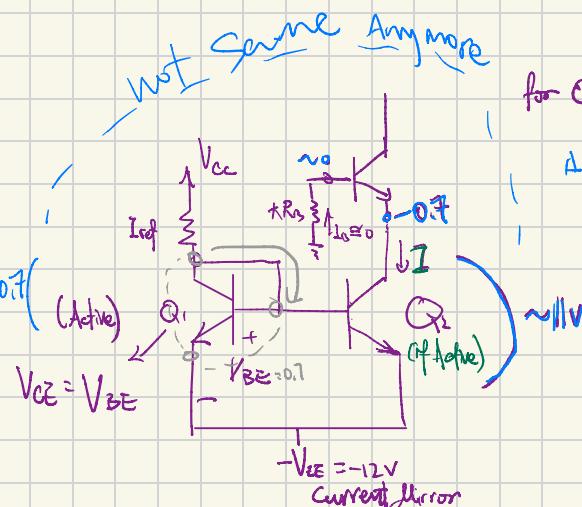
$$\frac{I}{I_{ref}} = \frac{1}{1 + 2\frac{1}{\beta}}, \text{ if } \beta \gg 2 \Rightarrow I \approx I_{ref}$$



for Q_1 , $V_{ce} = V_{be}$

$\Delta I = \frac{11 - 0.7}{R_0}$ 电压 slope


$I = I_{ref} + \Delta I \leftarrow \text{(considering Early effect)$

① $I_c = I_s e^{V_{BE}/V_t}$

$\therefore V_{BE}$ 一样 (BJT 一样)

§ 5.6 Small-Signal operation of models

Timode CE

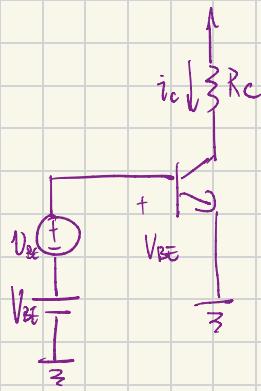

amplification (Active)

$$i_c = I_s e^{\frac{V_{be} + v_{be}}{V_t}} = I_s e^{\frac{(V_{be} + v_{be})}{V_t}} = I_s e^{\frac{V_{be}}{V_t}} e^{\frac{v_{be}}{V_t}}$$

$$i_c \underset{\text{DC}}{\approx} I_s e^{\frac{V_{be}}{V_t}}$$

$$= I_c \left(1 + \frac{V_{be}}{V_t} \right) \quad \begin{matrix} \text{Small signal} \\ \text{Approximation} \end{matrix}$$

$$\downarrow \quad V_{be} \ll V_t \quad (V_{be} \leq 10 \text{ mV})$$

$$= I_c + \left(\frac{I_c}{V_t} V_{be} \right) \quad \begin{matrix} \text{DC} \\ \text{忽略} \end{matrix} \quad \therefore \quad i_c = g_m V_{be}$$

$$i_c \underset{\text{AC}}{\approx} g_m V_{be}$$

$$g_m \equiv \frac{I_c}{V_t}$$


(transconductance)

AC 信号
放大系数

e.g. for $I_c = 1 \text{ mA}$, $g_m = 40 \text{ mA/V}$ (电流放大)

(much larger than MOSFET)

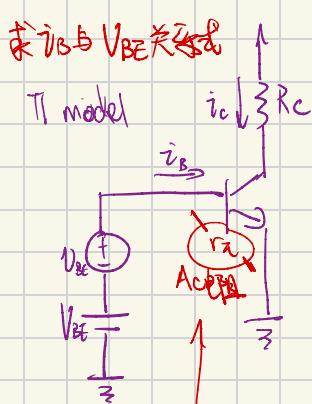However, In practical, we have consider R (高增益一般都有配用阻抗)




$$i_b = \frac{i_c}{\beta} = \frac{1}{\beta} (I_c + i_c) = \frac{I_c}{\beta} + \frac{g_m}{\beta} V_{be}$$

$$\frac{i_b}{i_c}$$

input 串联电极电阻

② high- π model (small signal)

输出端有反馈

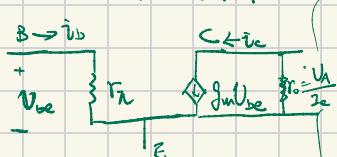

$$i_b = \frac{g_m}{\beta} V_{be}$$

$$\boxed{\text{Define: } r_{in} \equiv \frac{V_{be}}{i_b} = \frac{\beta}{g_m}}$$

(AC 电阻)


$$r_{in} = \frac{\beta}{\frac{I_c}{V_t}} = \frac{V_t}{\left(\frac{I_c}{\beta} \right)} = \frac{V_t}{I_\beta}$$

② high- π model (small signal)

starts from π model

π -model

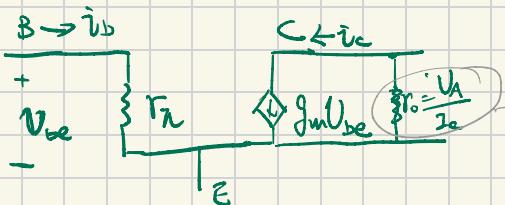Input i_{be} at \bar{V}_B , i_{ce} current



consider Early Voltage

$$i_c = \frac{V_A}{R_L} \quad R_o = \frac{V_A}{i_c}$$

$\S \pi$ -model


input i_{be} to \bar{V}_B

i_{ce} current

$$\bar{V}_{ce} = \bar{V}_{ce} + \bar{i}_b = g_m V_{be} + \frac{V_{be}}{r_n} = \left(g_m + \frac{1}{r_n} \right) V_{be}$$

$$\text{Define: } r_e = \frac{V_{be}}{i_e} = \frac{1}{g_m + \frac{1}{r_n}} = \frac{r_n}{1 + g_m r_n} = \frac{r_n}{\beta} = \frac{V_t}{(1+\beta) I_B} = \frac{V_t}{I_B}$$

π -model

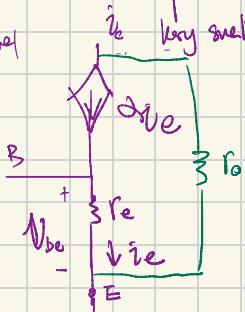


$$r_e = \frac{V_t}{I_B}$$

$$g_m = \frac{\beta}{r_n}$$


$$r_\pi = \frac{V_t}{I_B}$$

\S Eq. 5.14
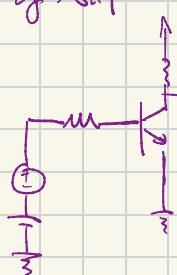
$$V_{cc} = 10V \quad \beta = 100 \quad \text{find } \frac{V_o}{V_{ib}}$$



π -model

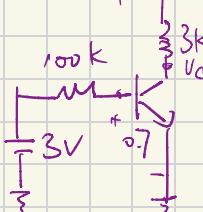

$$I_B = \frac{3.07}{100} = 0.0307mA$$

$$I_C = \beta I_B = 2.3mA$$


$$V_C = 10 - 2.3 \times 3 = 3.1V$$

c-BJ reverse bias \rightarrow Active

$$g_m = \frac{I_c}{V_t} = \frac{2.3}{0.025} = P_2 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{2.3} = 1.09 \text{ k}\Omega$$

Ac Signal:

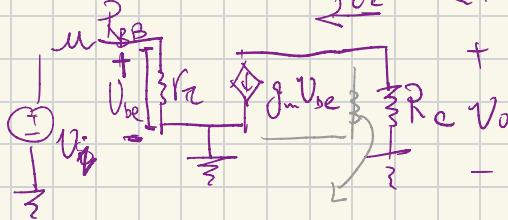

(Dc 电压源接地)

$$V_o = -i_c R_c = -g_m V_{BE} R_c$$

$$V_o = \frac{r_\pi}{R_{BB} + r_\pi} V_i$$

$$r_o = \frac{V_o}{i_c} = \frac{23 \text{ V}}{2.3 \text{ mA}} = 10 \text{ k}\Omega$$

Answer:

$$\frac{V_o}{V_i} = -\frac{r_\pi}{R_{BB} + r_\pi + g_m R_C}$$


$$= -3.04 \text{ V/V (过大)}$$

问题： R_{BB} 太大， r_π 太小，增益过大

(P3)

§ Small-Signal Model

π -model

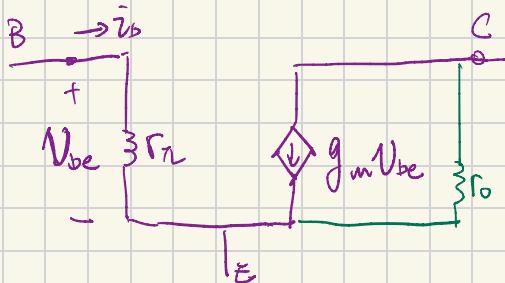

$$i_c = I_s e^{V_{BE}/V_T}$$


$$g_m = \left. \frac{\partial i_c}{\partial V_{BE}} \right|_{I_C} = \frac{I_c}{V_t} \Rightarrow i_c = g_m V_{BE}$$

$$r_\pi = \frac{V_t}{I_S}$$

$$\text{if } \text{neg } r_o = \frac{V_A}{I_C}$$

在此 AC model 中，虽然 AC current 方向不同
但在此只假设一个方向

T model

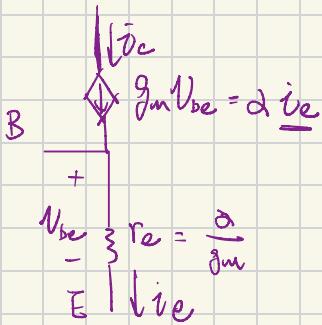


$$r_e = \frac{V_T}{1 + \beta} = \frac{V_T}{I_E}$$

$$\alpha V_{be} = \alpha \frac{V_{be}}{r_e} \Rightarrow \frac{1}{r_e} = \frac{\alpha}{\alpha + 1}$$


$$r_e = \frac{\alpha}{\alpha + 1}$$

Eq. 5.16

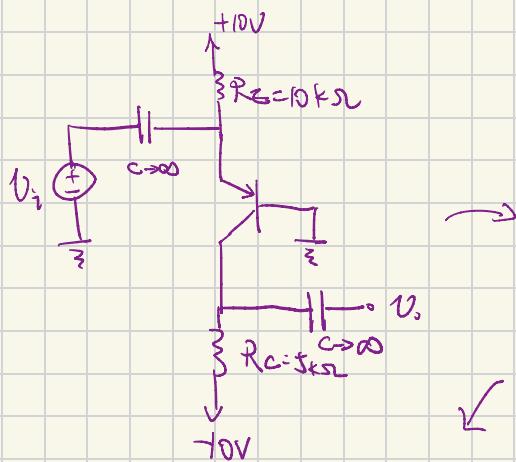

DC:

PNP

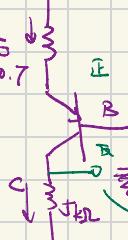

$$\alpha = 0.99 \quad \beta = 100$$

$$I_E = \frac{10 - 0.7}{10} = 0.93 \text{ mA}$$


$$I_C = 0.93 \text{ mA}$$

$$P = 0.9 \times 5 - 10 = -5.4 \text{ V}$$

$$V_D > 0.54 \text{ V} \rightarrow \text{active}$$

* AC
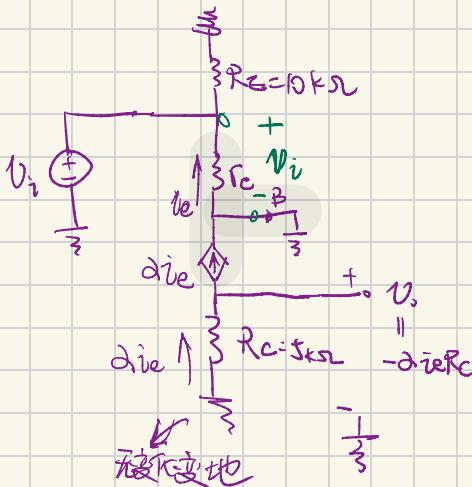
$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.93 \text{ mA}} = 27 \Omega$$



$$i_{ce} = -\frac{V_o}{r_e}$$



$$V_o = -\alpha \left(-\frac{V_o}{r_e} \right) R_C$$

$$\frac{V_o}{V_i} = \alpha \frac{R_C}{r_e} = 1.833 \text{ V/V}$$

$i_{ce} = -\frac{V_o}{r_e}$
 $V_o = -\alpha \left(-\frac{V_o}{r_e} \right) R_C$

[Collect \rightarrow Emitter bias - 3k]

Small Signal Approximation

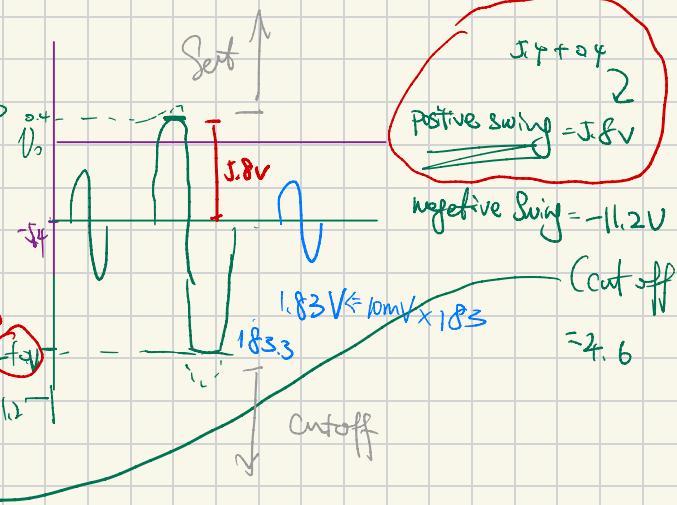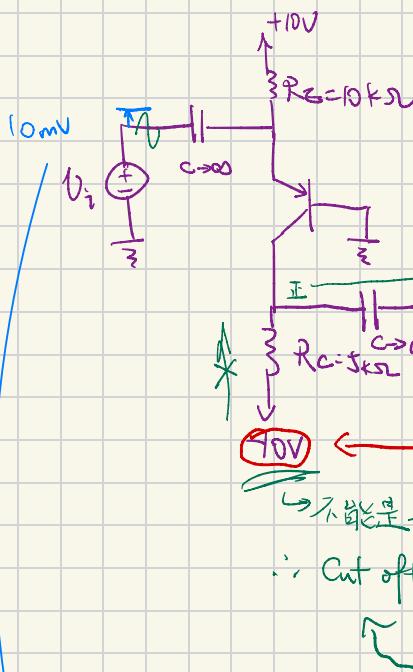

$$i_c = I_s e^{(V_{BE} + V_{BC})/V_t} = I_s e^{V_{BE}/V_t} e^{V_{BC}/V_t} \approx I_s \left(1 + \frac{V_{BE}}{V_t}\right)$$

适用于 $|V_{BE}| < 1$, 2次方项忽略


Consider the linearity
of small signal, not linear




$V_{BE} \ll V_t$
 $V_{BE} \leq 10\text{mV}$

(4-4) Single-stage BJT amplifiers


AC signal + DC

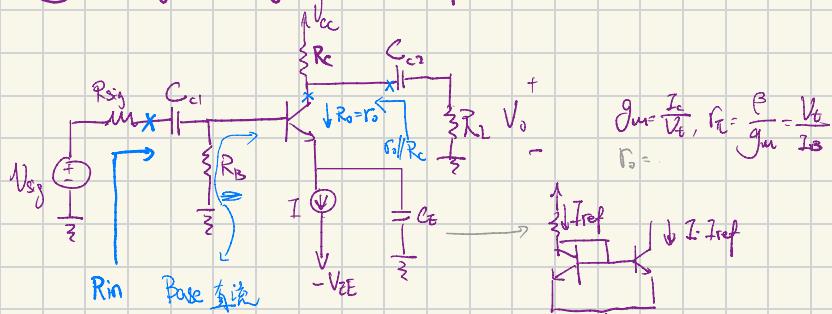
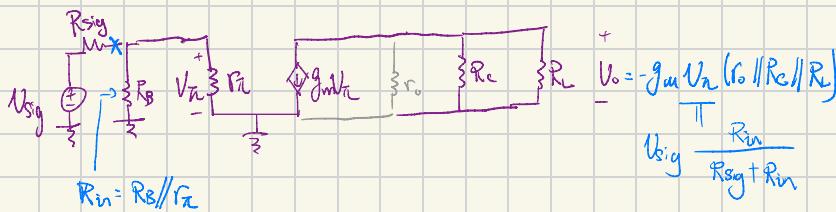
$$g_{m1} = \frac{I}{V_B}, R_L = \frac{\beta}{g_{m1}} = \frac{V_B}{I}$$



the CE with RC

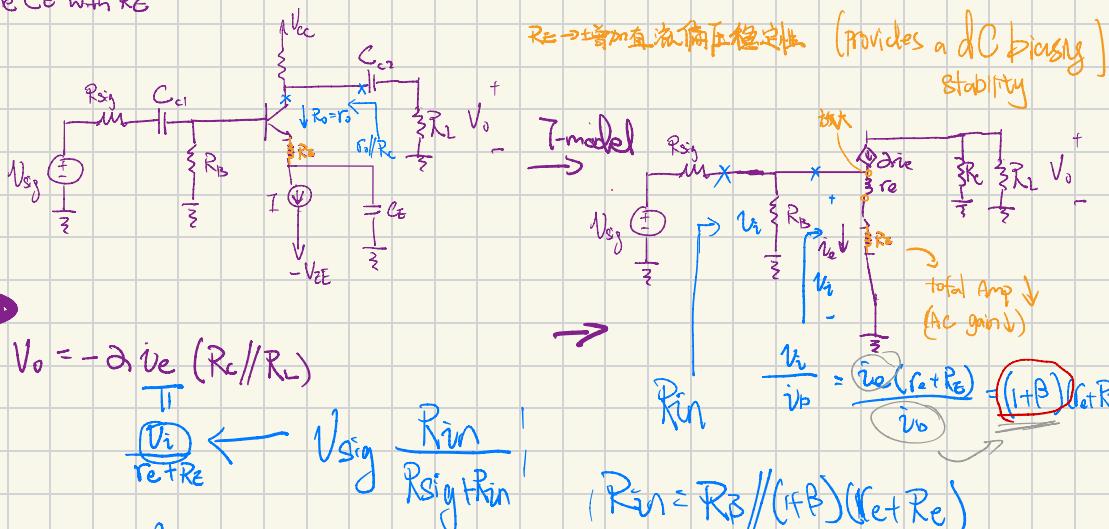


$$V_0 = -\alpha \cdot i_e (R_C // R_L)$$

$$\frac{V_0}{V_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}}$$


$$\Rightarrow \frac{V_0}{V_{sig}} = -\alpha \frac{(R_C // R_L)}{R_{in} + R_E} \cdot \frac{R_{in}}{R_{sig} + R_{in}}$$

total
Amplifier

$$|R_{in}| = R_B // (f\beta) (R_E + R_E)$$

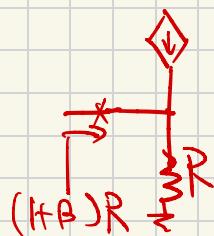


§ the CB

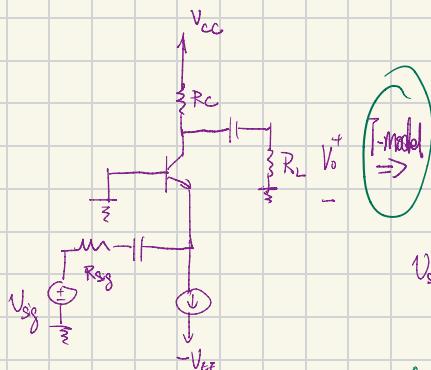

↳ Current ~~path~~, unity-gain
Current Amplifier

neglect r_o

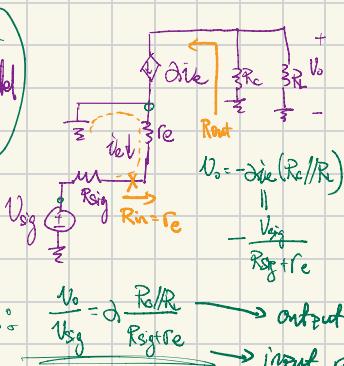

$$\therefore r_e = \frac{V_T}{1+\beta} = \frac{V_T}{Z_L}$$

$$r_\pi = \frac{V_T}{I_C} \sim kT/k$$

$\therefore R_{in} = r_e$

Very small


$R_{out} \gg$ very big

↳ R_{sig} & R_{out} (Perfect current amplifier)
 low input resistance
 high output resistance



(45)

5.7.6 The CC

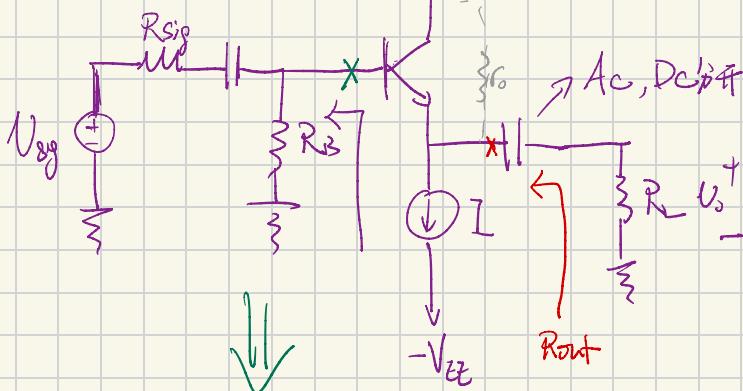

Ac $\xrightarrow{\text{共集电极}}$ (Common Collector)
 in $\xrightarrow{\text{B}} \text{E}$ out

Ac, Dc $\xrightarrow{\text{共集电极}}$


T -model

Emitter follower (Voltage gain = 1)

relatively high input resistance

$$V_o = V_i - \frac{(r_o // R_L)}{R_e + (r_o // R_L)} \approx V_i$$
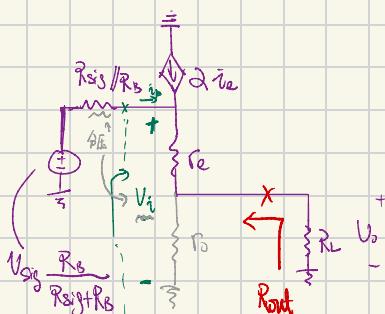
$$\frac{V_o}{I_o} \Rightarrow \text{very small}$$



$$R_{in} = \frac{V_{in}}{I_B} = \frac{(V_{sig} + I_B R_s)}{I_B}$$

$$= (R_s + (r_o // R_L)) (1 + \beta)$$


$$V_{in} = V_{sig} - \frac{R_B}{R_{sig} + R_B} \cdot \frac{(1 + \beta)(r_o + r_{o'}/R_L)}{(R_{sig}/R_B) + (1 + \beta)(r_o + r_{o'}/R_L)}$$

Substitute V_o


$$\therefore \frac{V_o}{V_{sig}} = \frac{R_B}{R_{sig} + R_B} \times \frac{(1 + \beta)(r_o // R_L)}{(R_{sig} // R_B) + (1 + \beta)(r_o + r_{o'}/R_L)} \approx 1$$

$$= \frac{R_B}{R_{sig} + R_B} \times \frac{(r_o // R_L)}{\frac{(R_{sig} // R_B)}{1 + \beta} + (r_o + r_{o'}/R_L)} \approx 1$$

R_B 取很大

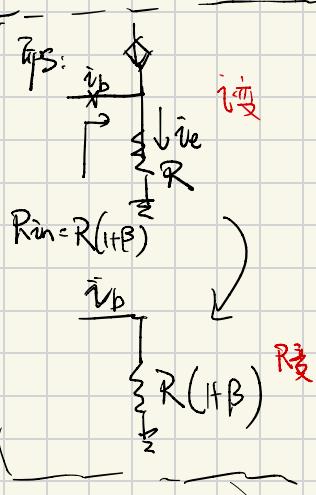

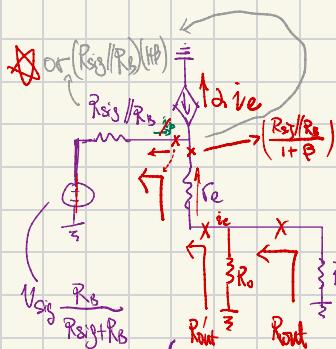\rightarrow \rightarrow \rightarrow \rightarrow




$$R_{out}' = \frac{R_{sig} // R_B}{1 + \beta} + r_e$$


$$R_{out} = \left(\frac{R_{sig} // R_B}{1 + \beta} + r_e \right) // r_o$$

Very small

A very small output resistance


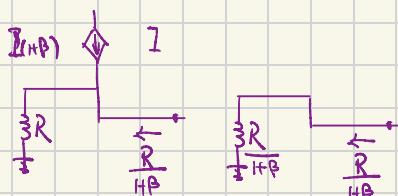


等效模型

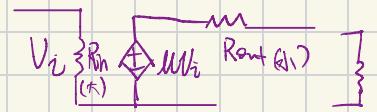


DC/AC电压导通

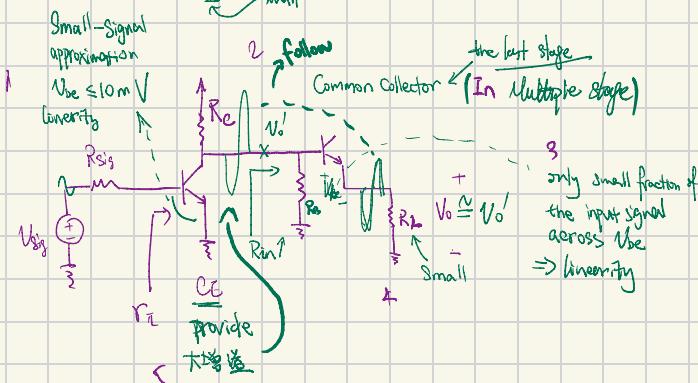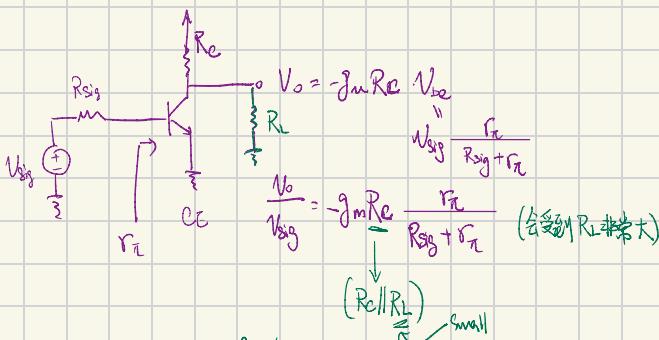Perfect Voltage Amp (Ideal)
(信号源 & L影响较小)
 $V_{in} \rightarrow V_{out}$



分析 (大R, 小R)

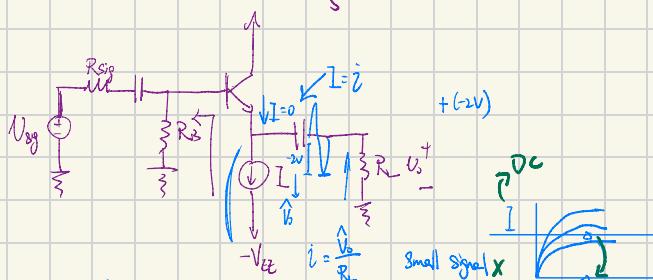


DC放大AC电压影响

$I < \text{small signal} \Rightarrow \text{Cut off}$

The peak output voltage $\hat{V}_o = I R_L$

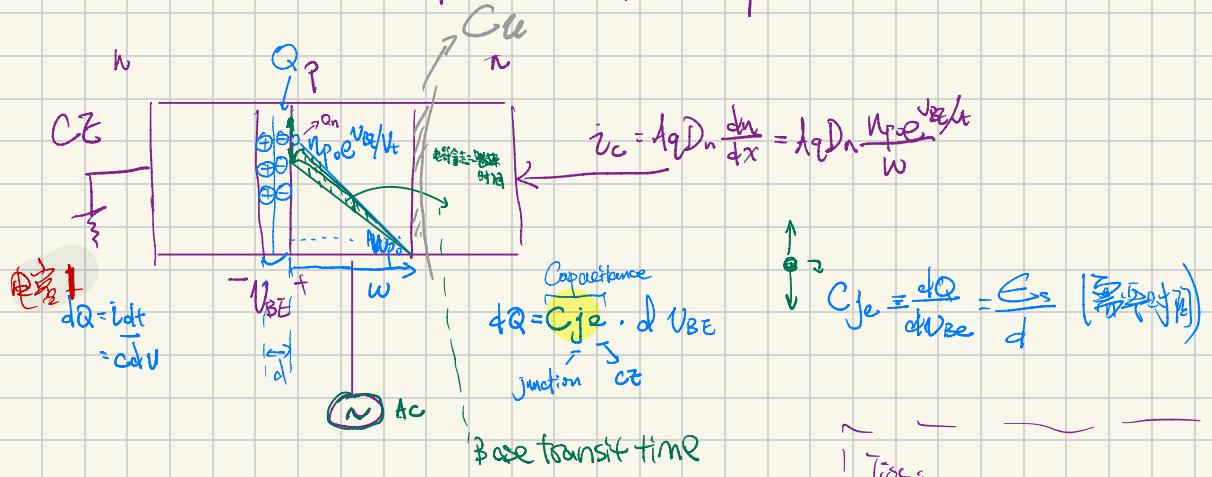§ 5.8. The BJT Internal Capacitances of High-f Mode



$$Q_n = A \frac{1}{2} q n_{p0} e^{V_{BG}/V_t} \frac{w^2 D_n}{w D_n} = i_c \left(\frac{w^2}{2 D_n} \right)$$

电容 2
Forward

$$dQ_n = I_F \cdot d i_c = I_F g_m d V_{BE} \Rightarrow i_c = g_m V_{BE}$$

$$C_{de} = \frac{dQ_n}{dV_{BE}} = I_F g_m$$

Total: $dQ = dQ + dQ_n$


$$= C_{je} \cdot d V_{BE} + C_{de} \cdot d V_{BE}$$

$$= (C_{je} + C_{de}) \cdot d V_{BE}$$


并联

1. 电流：电荷对时间的变化
 2. 通过用时
 $\Rightarrow Q/I = t$
 $Q/I = I$

Model

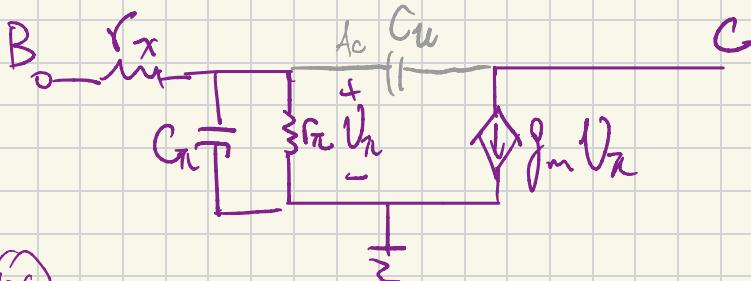


(P6)

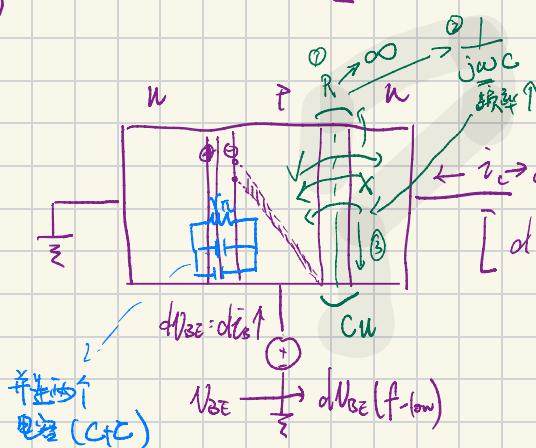

$$\text{Total } dQ = dQ_n + dQ_p \\ = \frac{(C_{je} + C_{de})}{C_{in}} dV_{BE}$$


$$dQ = C_{je} dV_{BE}, \quad dQ_n = \frac{C_{de}}{C_{in}} dV_{BE}$$
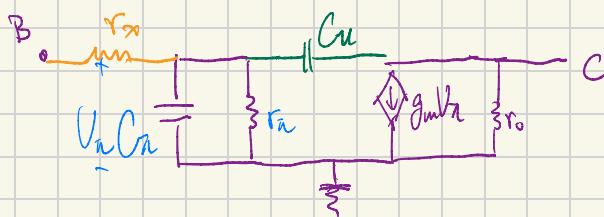
$$\text{base transit time} \\ T_F = \frac{w}{2D_n} \approx \tau_p$$



§ A figure of merit

CE short-circuit current gain

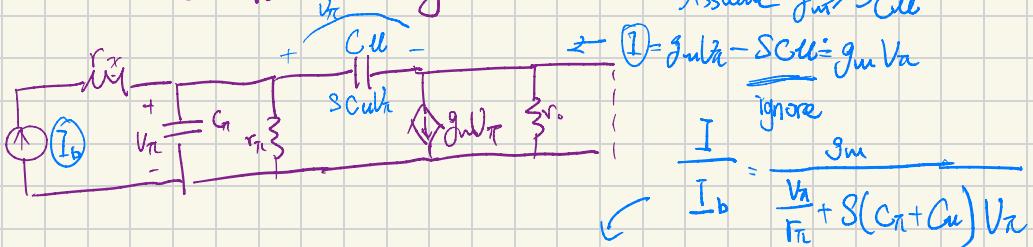

$$\text{assume } g_m \gg S C_{in}$$

$$\textcircled{1} = g_m V_B - S C_{in} V_E = g_m V_B$$

Ignore

$$\frac{I}{I_B} = \frac{g_m}{\frac{V_B}{R_B} + S(C_B + C_E)V_E}$$

$$\left| \frac{I}{I_b} \right| = \frac{g_m f_{3dB}}{1 + Sf_x(C_n + C_u)}$$

$$f_{3dB} = \frac{W_{3dB}}{2\pi} = \frac{1}{2\pi f_x(C_n + C_u)}$$

$$f_t (\text{增益=1时}) = \frac{g_m f_x}{2\pi f_x(C_n + C_u)}$$

$$= \frac{g_m}{2\pi (C_n + C_u)}$$

Eg.

frequency response of the CB

